


# ECE 304 Spring '06: Lab 2

## Current Mirror Design Project

### Objective

To make a current mirror design tool and test one of its designs by building it.

### Schematic

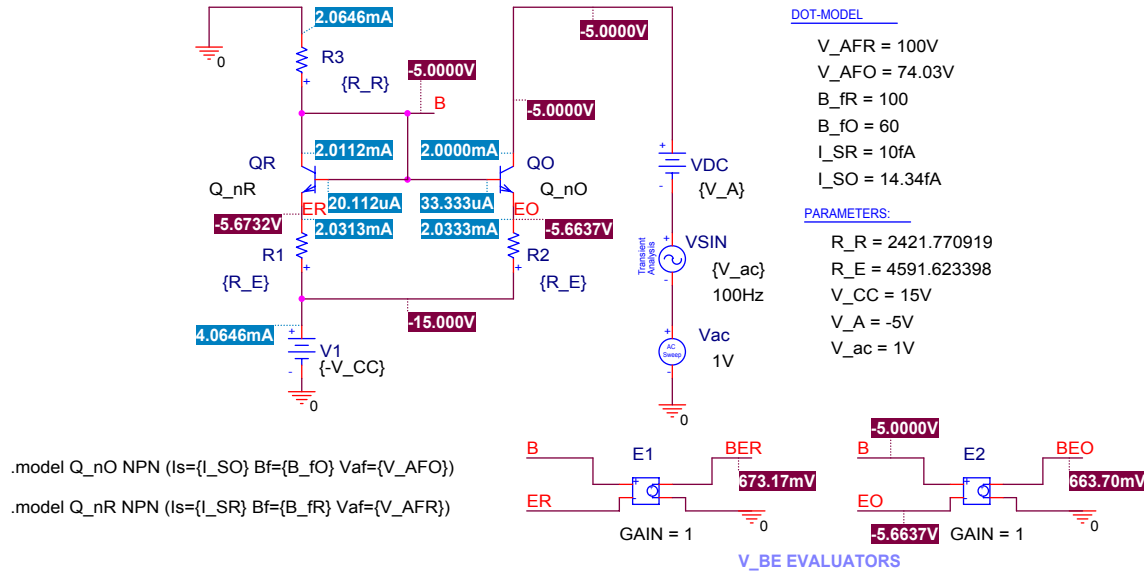

**FIGURE 1**

Schematic for current mirror with mismatched transistors

Figure 1 shows the circuit schematic and dot-model statements (repeated below for easy copying). At the bottom of the schematic are two evaluator circuits that have nothing to do with the current mirror operation, but display the base-emitter voltages for comparison with the spreadsheet. The evaluators make it unnecessary to mentally subtract two voltages on the schematic itself.

### Dot-model statements

```
.model Q_nR NPN (Is={I_SR} Bf={B_FR} Vaf={V_AFR})
.model Q_nO NPN (Is={I_SO} Bf={B_FO} Vaf={V_AFO})
```


**FIGURE 2**

Dot-model statements for ideal mismatched transistors; you will use the parameters you measured for your Q2N2222 transistors

### Specifications

The specifications could involve any of the following properties, illustrated with the example of Figure 1.


1. A maximum output voltage swing that the mirror will be subjected to, say  $V_{ac}$ . Under these conditions, the output current from a transient simulation using a sinusoidal output voltage superposed on the DC background is shown in Figure 3. The upward blip in current shows that the mirror is on the edge of going into the low Norton resistance region at this AC voltage. The upward spike increases rapidly as  $V_{ac}$  is increased.

 

**FIGURE 3**

Transient mirror current for set-up of Figure 1 for  $V_{ac} = 5\text{ V}$  and  $5.5\text{ V}$ , and  $V_A = 0\text{ V}$


2. A DC current level the mirror produces when  $V_A = V_B$ . Figure 1 produces about  $2\text{ mA}$  for voltages above the compliance voltage.
3. A compliance voltage  $V_{CV}$  that specifies how low the DC voltage across the mirror can be and still have a DC output current of  $I_o$ . In Figure 4 we see the mirror of Figure 1 has a compliance voltage of about  $V_{CV} = -5\text{ V}$ .

 

**FIGURE 4**

DC I-V plot for mirror of Figure 1 showing delivered DC output current of  $I_o = 2\text{ mA}$  for  $V_A = V_B = -5\text{ V}$ ; the compliance voltage is slightly lower at  $V_{CV} = -5.58\text{ V}$

4. A maximum AC ripple current that should result when the maximum swing is present,  $V_{ac}/R_N$ , where  $R_N$  is the small-signal mirror resistance. Figure 3 shows the ripple as  $3\text{ }\mu\text{A}$  for a  $5\text{ V}$  swing. Figure 5 shows that  $R_N$  increases as  $R_E$  increases until, at  $R_E = 4.9\text{ k}\Omega$  the output transistor saturates forcing the mirror into the low resistance regime, where  $R_N$  drops abruptly. As long as  $R_N$  increases with  $R_E$ , the AC ripple current  $V_{ac}/R_N$  will drop as  $R_E$  is increased.

 

**FIGURE 5**


Dependence of mirror Norton resistance  $R_N$  upon value of leg resistor  $R_E$  for mirror of Figure 1

The specifications 1-4 above are interconnected, and only two independent requirements can be specified, because the mirror has only two independent parameters,  $R_E$  and  $R_R$ . For example,

specification of the DC mirror current at a specified applied voltage and simultaneous specification of the compliance voltage are sufficient to determine the design,.

### Design Tool


The design tool consists of a spreadsheet based upon formulas of a hand analysis and verified by PSpice simulations. The organization of the spreadsheet is shown in Figure 6.

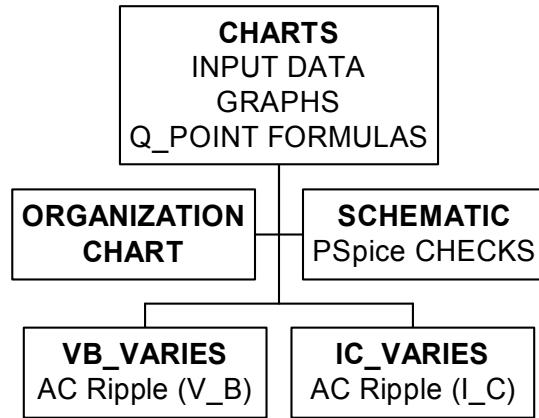

**FIGURE 6**

Organization of the worksheets in the spreadsheet

This flow chart is inserted on the worksheet ORGANIZATION using the menu INSERT/OBJECT and selecting MS ORGANIZATION CHART, as shown in Figure 7.

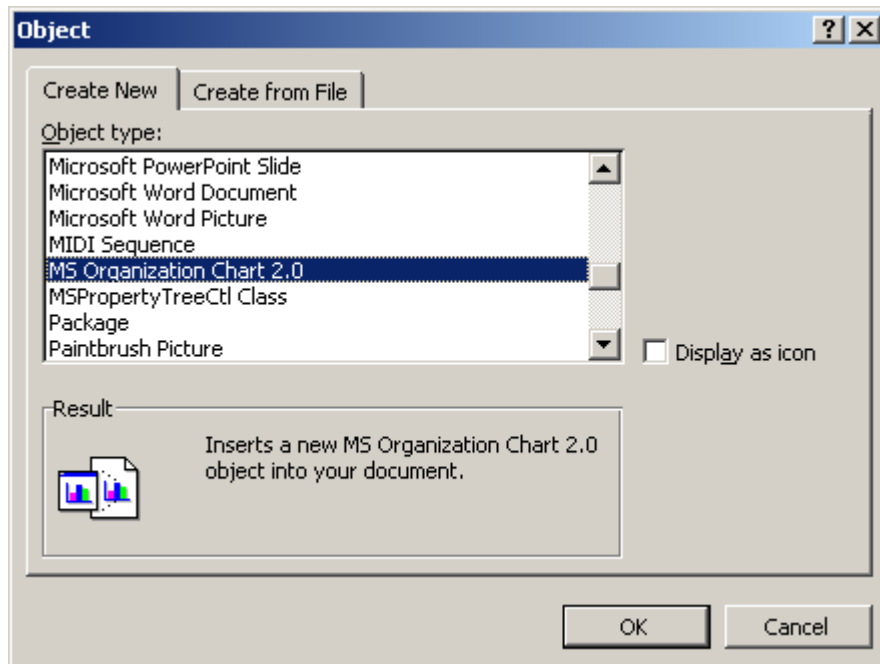

**FIGURE 7**

Inserting a flowchart into EXCEL

The other worksheets are shown below. Cells F8 and F9 on the CHARTS worksheet of Figure 8 below show that the base voltage  $V_B$  and the output current  $I_C$  in mA for  $V_A = V_B$  are chosen as the design variables. These two variables are chosen because they make the formulas simple for the rest of the design. The circuit design requires values for the resistors  $R_E$  and  $R_R$ , which are conveniently copied from the calculations into the DESIGN SUMMARY box. Regardless of which two

independent mirror properties from the previous list are specified, the spreadsheet enables selection of values of  $R_E$  and  $R_R$  that will meet the specifications.

	C	D	E	F	G
3				Design Summary	
4			$\Omega$	$R_R$ 2421.77092	
5	<b>CHARTS Worksheet</b>		$\Omega$	$R_E$ 4591.6234	
6	Design assumes $V_A = V_B$				
7					
8	Input	Base voltage	V	$V_B$	-5
9		Mirror current @ $V_A=V_B$	mA	$I_C(\text{mA})$	2
10		AC input voltage amplitude	V	$V_{AC}$	1
11		Supply voltage	V	$V_{CC}$	15
12		Thermal voltage	V	$V_{TH}$	0.025864
13					
14	Dot-Model	Early voltage (ref)	V	$V_{AFR}$	100
15		Early voltage (out)	V	$V_{AFO}$	74.03
16		DC beta @ $V_{CB}=0$ (ref)		$B_{DCR}$	100
17		DC beta @ $V_{CB}=0$ (out)	A/A	$B_{DCO}$	60
18		AC beta @ $V_{CB}=0$ (ref)	A/A	$B_{ACR}$	100
19		AC beta @ $V_{CB}=0$ (out)	A/A	$B_{ACO}$	60
20		Scale current (ref)	A	$I_{SR}$	1.000E-14
21		Scale current (out)	A	$I_{SO}$	1.434E-14
22					
23	Calculated	Change units	A	$I_C$	0.002
24		Output emitter-base V	V	$V_{BEO}$	0.66369909
25		Leg resistor	$\Omega$	$R_E$	4591.6234
26	Iteration for $I_{CR}$ and $V_{BER}$	Initial guess	V	$V_{BER1}$	0.7
27				$I_{CR1}$	0.00200537
28				$V_{BER2}$	0.67309163
29				$I_{CR2}$	0.00201118
30				$V_{BER3}$	0.67316635
31				$I_{CR3}$	0.00201116
32				$V_{BER4}$	0.67316615
33				$I_{CR4}$	0.00201116
34				$V_{BER5}$	0.67316615
35				$I_{CR5}$	0.00201116
36		Emitter-base V		$V_{BER}$	0.67316615
37		Ref Transistor IC		$I_{CR}$	0.00201116
38		Reference resistor	$\Omega$	$R_R$	2421.77092
39					
40	AC ripple current	NPN base resistance	$\Omega$	$r_{PIR}$	1286.02403
41		NPN base resistance	$\Omega$	$r_{PIO}$	775.92
42		Emitter current (ref)	A	$I_{ER}$	0.00203127
43		NPN ref emitter resistance	$\Omega$	$r_{ER}$	12.7329112
44	$V_{ac}$ sine wave at output	$R_R/(r_{ER}+R_E)$	$\Omega$	$R_{EFF}$	1587.03306
45		NPN output resistance	$\Omega$	$r_O$	37015
46		Small-signal mirror R	$\Omega$	$R_N$	1.507E+06
47		Output current ripple	$\mu\text{A}$	$I_{AC}(\mu\text{A})$	0.66362959
48					
49	Cross check	Leg resistor (ref)	$\Omega$	$R_E$	4591.6234
50		Compare with output side value		% Error	1.9808E-14

**FIGURE 8**

Layout of CHARTS worksheet including hand analysis formulas for the mirror at  $V_A = V_B$ , that is, for the case where  $V_{CB} = 0$  V for both transistors

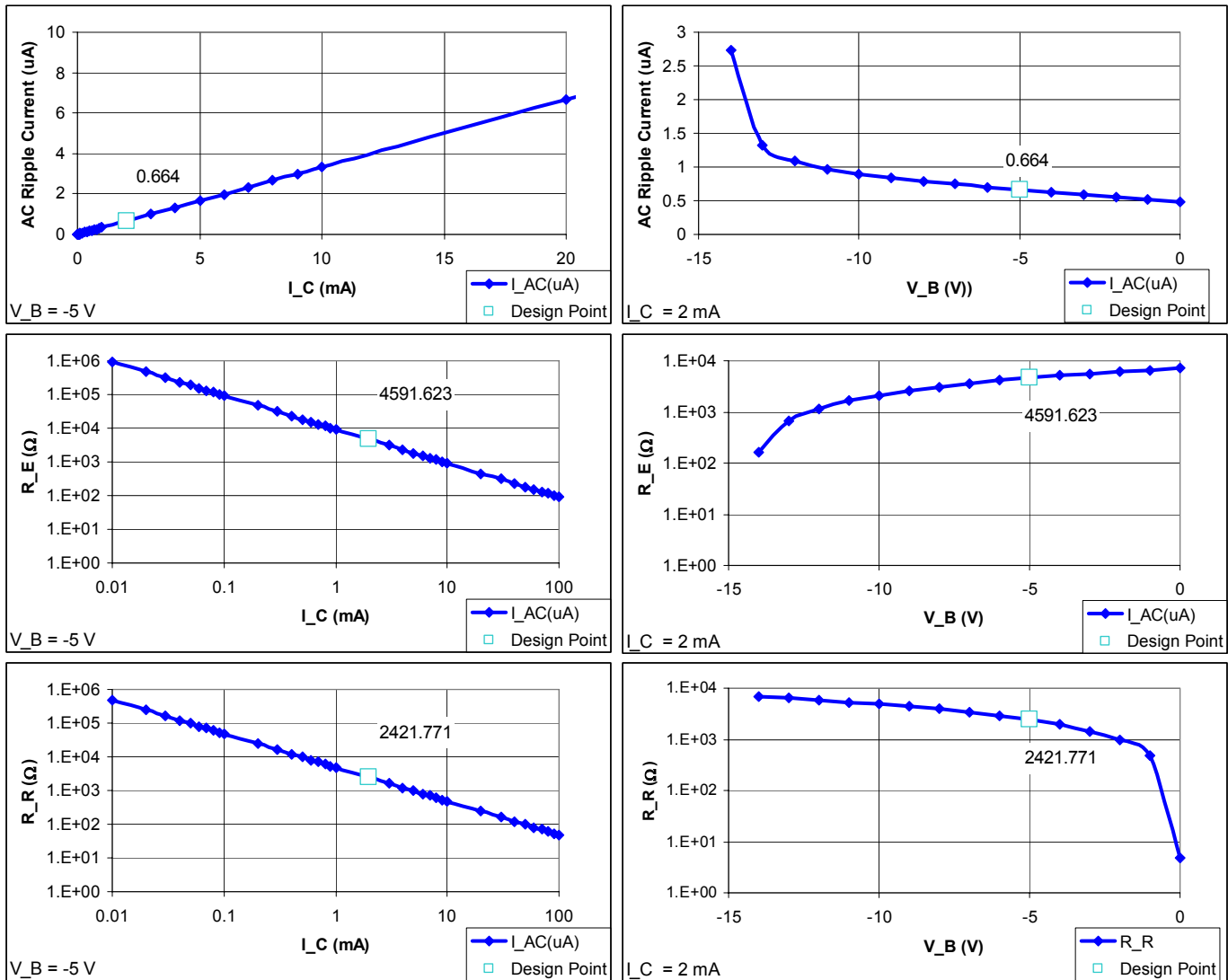


FIGURE 9

Charts on the CHART worksheet; the calculations are done on worksheets IC\_VARIES and VB\_VARIAS

I_CR1		=(V_CC+V_B-V_BER1)/(R_E*(1+1/B_DCR))														
C	D	E	F	T	U	V	W	X	Y	Z	AA	AB	AC	AD	AE	AF
5	IC_VARIAS Worksheet															
6	Label V_B = -5 V															
7																
8		V_B	I_C(mA)	I_C	V_BEO	R_E	V_BER1	I_CR1	V_BER2	I_CR2	V_BER3	I_CR3	V_BER4	I_CR4	V_BER5	I_CR5
9		-5	0.01	0.00001	0.526663	931803.6	0.7	9.88E-06	0.535679	1.01E-05	0.536132	1.01E-05	0.536131	1.01E-05	0.536131	1.01E-05
10			0.02	0.00002	0.544591	465020.1	0.7	1.98E-05	0.553656	2.01E-05	0.554059	2.01E-05	0.554058	2.01E-05	0.554058	2.01E-05
11			0.03	0.00003	0.555078	309669.6	0.7	2.97E-05	0.564171	3.02E-05	0.564546	3.02E-05	0.564545	3.02E-05	0.564545	3.02E-05
27			1	0.001	0.645772	9200.88	0.7	0.001001	0.655114	0.001006	0.655239	0.001006	0.655239	0.001006	0.655239	0.001006
28			2	0.002	0.663699	4591.623	0.7	0.002005	0.673092	0.002011	0.673166	0.002011	0.673166	0.002011	0.673166	0.002011
29			3	0.003	0.674186	3057.644	0.7	0.003011	0.683608	0.003017	0.683653	0.003017	0.683653	0.003017	0.683653	0.003017
30			4	0.004	0.681627	2291.403	0.7	0.004018	0.691069	0.004022	0.691094	0.004022	0.691094	0.004022	0.691094	0.004022

FIGURE 10

Segment of IC\_VARIAS worksheet; first iteration for I\_CR is in FORMULA BOX

The IC\_VARIAS worksheet is formed by copying columns F and G on CHARTS and using menu PASTE SPECIAL/TRANSPOSE to paste these columns as rows on a new worksheet. Then a column of values is entered for the variable to be varied, I\_C in this case, and this column is named using INSERT/NAME/CREATE. Then the calculated variable formulas are filled in under their column

headings using the cursor. The cursor is dragged to the corner of the cell until it becomes a plus sign, and then it is dragged down the column holding down the left mouse button, as shown in Figure 11 below.

= -V_B/(I_CR*(1+1/B_DCR)+I_C/B_DCO)			
AF	AG	AH	AI
I_CR5	V_BER	I_CR	R_R
1.01E-05	0.536131	1.01E-05	484347.2
2.01E-05	0.554058	2.01E-05	242174.1

**FIGURE 11**

Using the cursor to fill in a column of formulas, in this case R\_R

All the columns can be done at once. However, only the CALCULATED variables should be filled in. Columns T to AR are named using INSERT/NAME/CREATE. COLUMN AT is not named, because that would conflict with COLUMN V. COLUMNS F to R are not filled in and are not named, because we want the input data values to come from the entries on worksheet CHARTS, and do not want them replaced by values on this worksheet.

Label =CONCATENATE("I_C = "I_C_mA," mA")																
C	D	E	F	AI	AJ	AK	AL	AM	AN	AO	AP	AQ	AR	AS	AT	AU
5	VB VARIES Worksheet															
6	Label	I_C = 2 mA														
7																
8		V_B	I_C(mA)	R_R	r_PIR	r_PIO	I_ER	r_ER	R_EFF	r_O	R_N	I_AC(uA)		R_E	% Error	
9		-14	2	6953.347	1319.268	775.92	0.00198	13.06206	173.9905	37015	3.665E+05	2.728494		165.3939	2.06E-13	
18		-5		2421.771	1286.024	775.92	0.002031	12.73291	1587.033	37015	1.507E+06	0.66363		4591.623	1.98E-14	
19		-4		1937.23	1285.898	775.92	0.002031	12.73166	1403.652	37015	1.596E+06	0.626747		5083.427	0	
20		-3		1452.807	1285.794	775.92	0.002032	12.73064	1153.032	37015	1.692E+06	0.591104		5575.23	1.63E-14	
21		-2		968.4737	1285.707	775.92	0.002032	12.72978	835.3991	37015	1.797E+06	0.556402		6067.033	1.5E-14	
22		-1		484.2094	1285.633	775.92	0.002032	12.72904	450.9801	37015	1.914E+06	0.522434		6558.837	1.39E-14	
23		-0.01		4.841861	1285.57	775.92	0.002032	12.72842	4.838542	37015	2.043E+06	0.48938		7045.722	0	

**FIGURE 12**

Segment of VB\_VARSIES worksheet, made the same way as IC\_VARSIES; the CONCATENATE function is used to make a label for the lower left corner of the charts, as seen in Figure 9

## Discussion

The transistor parameters are labeled with R for reference transistor and O for output transistor. The spreadsheet is set up with equations based on ideal transistors. Example dot-model statements for such transistors are shown in Figure 2, and these transistors are used to verify the spreadsheet by checking against PSPICE.

## Verification of spreadsheet

The spreadsheet is verified by running a schematic at the Q-point and comparing with the spreadsheet Q\_point currents and voltages and also by running curves like Figure 4 and Figure 5 and using a table to compare several points on each PSPICE curve with the spreadsheet.

## Specifications

Using your Q2N2222 transistor parameters, design a mirror using your EXCEL tool to meet these specifications:

- Supply voltage is  $V_{CC} = 6$  V.
- Resistor values for  $R_E$  are nominal 10% values. Actual values can vary from 10% above to 10% below nominal value and circuit still will meet specs.  $R_R$  is a pot.
- Lowest DC output current at  $V_{CB}(Q_0) = 0$  V is  $I_o = 10$  mA.
- Worst case AC ripple current is 37  $\mu$ A for 4.5 V AC swing.
- Choose the most favorable placement of transistors; for example, maybe it is best to put your highest  $\beta$  or your highest  $V_{AF}$  transistor as the output transistor. Use the spreadsheet to find the best arrangement.
- Determine the best  $V_{CV}$  for the mirror. Assume  $V_{CV} = V_B - 0.5$  V and find best  $V_B$ .
- Spreadsheet verification is as in the section VERIFICATION OF SPREADSHEET

## Prelab

1. Derive the equations needed for the spreadsheet using mismatched transistors.
2. Set up the spreadsheet and test it. Paste figures like those shown here in your lab notebook.
3. Tabulations of the comparisons between spreadsheet and PSPICE should be provided for bias point currents and voltages (for example,  $V_{BE}$ -values and  $I_C$  values) and small-signal parameters ( $r_{\pi}$ 's and  $r_o$ 's and  $\beta$ 's from OUTPUT FILE) for a spec of your choice.
4. Explain qualitatively the trends seen in the six graphs of the CHARTS worksheet. Put your explanations in the lab notebook.
5. Use your design tool to design to meet the specs of SPECIFICATIONS section using your measured Q2N2222 parameters and standard resistor values.
6. Verify your design by
  - 6.1. Showing DC I-V plots for highest and lowest value of  $R_E$  (that is, for nominal value  $\pm 10\%$ );  $V_{CV}$  and  $I$  should meet spec
  - 6.2. Showing spiking behavior like Figure 3 for highest and lowest  $R_E$ ; spiking should occur for an applied 4.5V swing only when DC  $V_A$  is set so the collector goes more than 0.5 V below the base.
  - 6.3. Also determine AC ripple currents for 4.5V swing from these plots.
  - 6.4. Tabulate your PSPICE results against the specs.

## Measurements

### PRECAUTION

Before using the signal generator, ask your TA how to put it in "high-Z" mode to protect the generator from burn-out.

The scope and meters can measure only voltages from a node to ground. You have to be careful in measuring an AC voltage that the instrument does not actually place the node you measure at DC ground, which can upset the bias of the circuit when the DC voltage of the node is not supposed to be at DC ground.

### MEASURING OUTPUT RESISTANCE

The output resistance of the mirror is very high, so it is hard to measure. Therefore, in the lab we will artificially assess the role of  $R_E$  in the mirror resistance by placing a known resistor value across the output transistor, artificially reducing its output resistance  $r_o$ . The setup is shown in Figure 13.


 


FIGURE 13

Set up to test output resistance formula

The 10F coupling capacitor should be sized smaller, as determined by a PSPICE simulation using a frequency sweep. The capacitor should be just large enough that C does not affect the measurement at the measurement frequency. Plots of mirror resistance vs. value of  $R_{TEST}$  should be made for three values of  $R_E$  and compared to PSPICE results, such as those in Figure 14 below.

 

**FIGURE 14**  
PSPICE determination of mirror resistance of circuit in Figure 13 for one value of  $R_E$  and  $V_A = 0$  V

The following questions should be answered:

1. What is the formula describing the mirror resistance for Figure 13?
2. Why is a coupling capacitor used in Figure 13?
3. How do your measured results for the mirror resistance compare with your formula – make a table of measured values and values from formula.

#### TASKS

1. The resistor values should be measured and tabulated in the notebook. Do not accept the color-code values.
2. When the circuit is built, the  $V_{BE}$  and  $V_{CB}$  values of both transistors should be measured and tabulated with the PSPICE results for comparison. All transistors should be in active mode.
3. Measure the DC I-V curve for your mirror, similar to Figure 4 and mark the coordinates at  $V_A = V_B$  and at the compliance voltage.
4. Put the signal generator between the output of the mirror and ground. Apply a sine wave voltage of amplitude  $V_{ac}$  and  $f = 500$  Hz. The signal generator allows both an AC voltage and an offset DC voltage to be applied. However, the amount of DC offset is a fraction of the AC amplitude: the larger the AC amplitude, the larger the allowed offset. The goal here is to choose a moderate AC amplitude that is large enough that the offset can be used to take the mirror above and below its compliance voltage, as shown by the spiking behavior illustrated in Figure 3. You can experiment to find a combination of  $V_{ac}$  and offset that works.
5. Tabulate your measured results alongside the PSPICE results and the specs.