

ECE 304 Fall '04 Final Exam

NOTE: IN ALL CASES

1. Put your answer first, and
2. Follow up with an outline of your solution. Each major step in the outline should
 - 2.1. Begin with a heading that describes the objective of that step, and should
 - 2.2. Have a body where actual work is done, not just hand waving, and should
 - 2.3. Conclude with a quantitative statement of the major result for that step (a number or formula or both).

For all problems take the thermal voltage as $V_{TH} = 25.864$ mV.

Problem 1: Current mirror

Follow the outline procedure at the top of the exam with headings for each major step in the solution. **No points for answer without an outline of the solution.**
A mish-mash of calculations is not an acceptable outline.

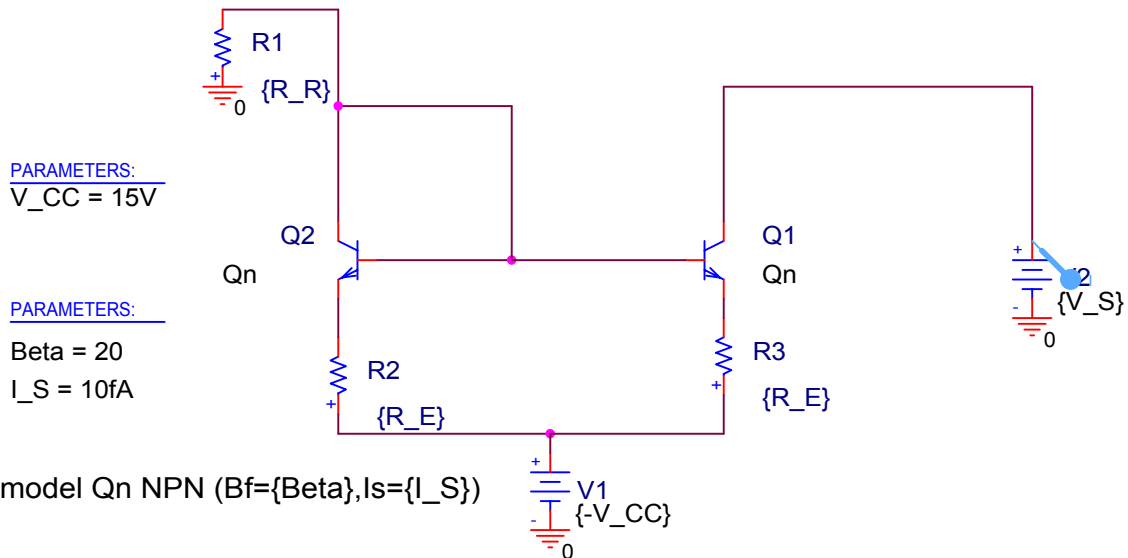


FIGURE 1
 Current mirror for Problem 1

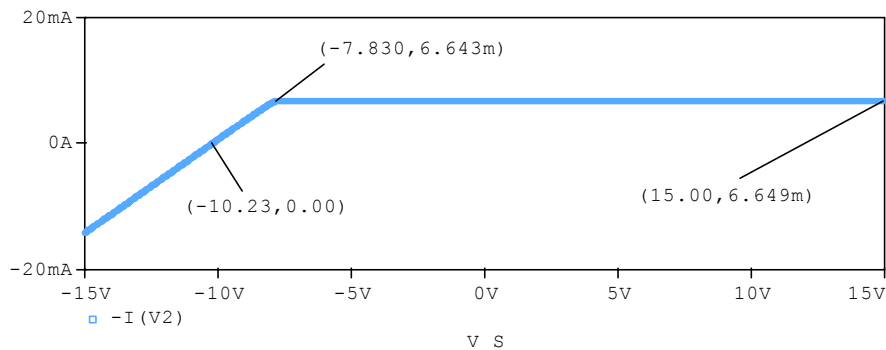


FIGURE 2
 Current vs. DC voltage for current mirror of Figure 1

Select values of R_R and R_E so the mirror will have the I - V behavior seen in Figure 2. Assume the maximum forward CB bias in saturation is $V_{CB} = -V_{SAT} = -500$ mV. Note that all transistors have infinite Early voltages.

Problem 2: Differential amplifier

Follow the outline procedure at the top of the exam with headings for each major step in the solution. **No points for answer without an outline of the solution.**
A mish-mash of calculations is not an acceptable outline.

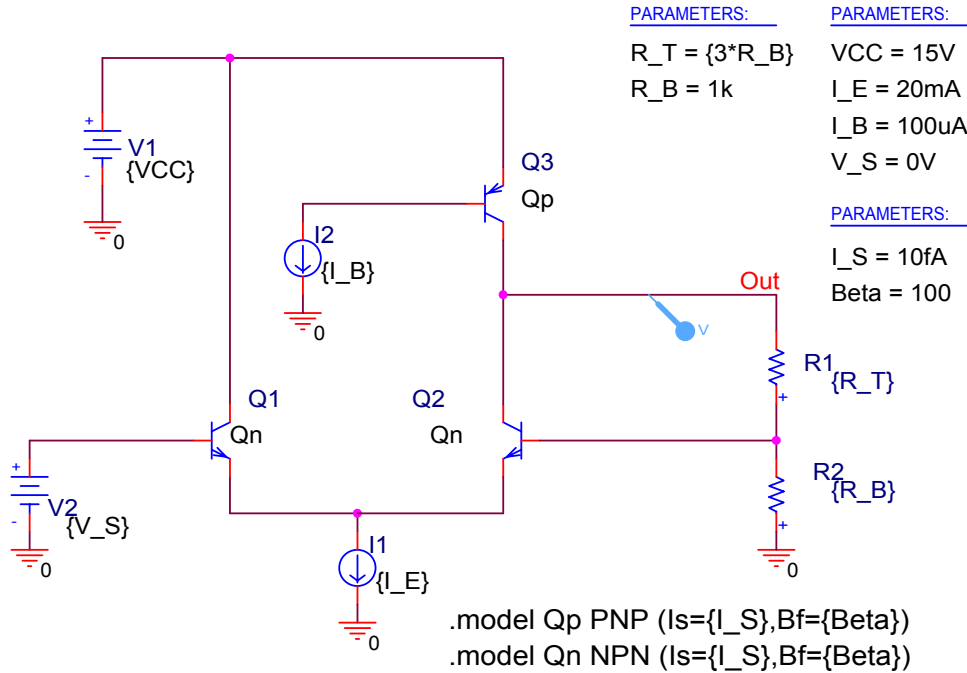


FIGURE 3
 Differential amplifier hooked up as a noninverting op amp

For the amplifier in Figure 3

1. Sketch four schematics, one for each of the cases $V_S = 10V, 2.5V, -5V$ and $-15V$. On each schematic label the modes of all transistors and the value of V_{OUT} .
2. Sketch the transfer curve V_{OUT} vs. V_S for $-15V \leq V_S \leq 15V$.
 - 2.1. Label all key break points with V_S - and V_{OUT} -coordinates.
 - 2.2. Label the slopes of all segments.
 - 2.3. Label the modes of all transistors in each segment of the transfer curve.

Assume the thermal voltage is $V_{TH} = 25.864$ mV. Assume the maximum forward CB bias is $V_{CB}(npn) = V_{BC}(pnp) = -V_{SAT} = 0$ V, and that in active mode $V_{BE}(npn) = V_{EB}(pnp) = 700mV$. Note that all transistors have infinite Early voltages.

Problem 3: Feedback

Follow the outline procedure at the top of the exam with headings for each major step in the solution. **No points for answer without an outline of the solution.**
A mish-mash of calculations is not an acceptable outline.

PARAMETERS:

$R_C = 800$

$R_L = 800$

$R_S = 800$

DOT-MODEL PARAMS


$I_S = 10\text{fA}$

$B_F = 100$

$C_{JC} = 2\text{pF}$

$C_{JE} = 2\text{pF}$

$T_F = 1\text{ns}$

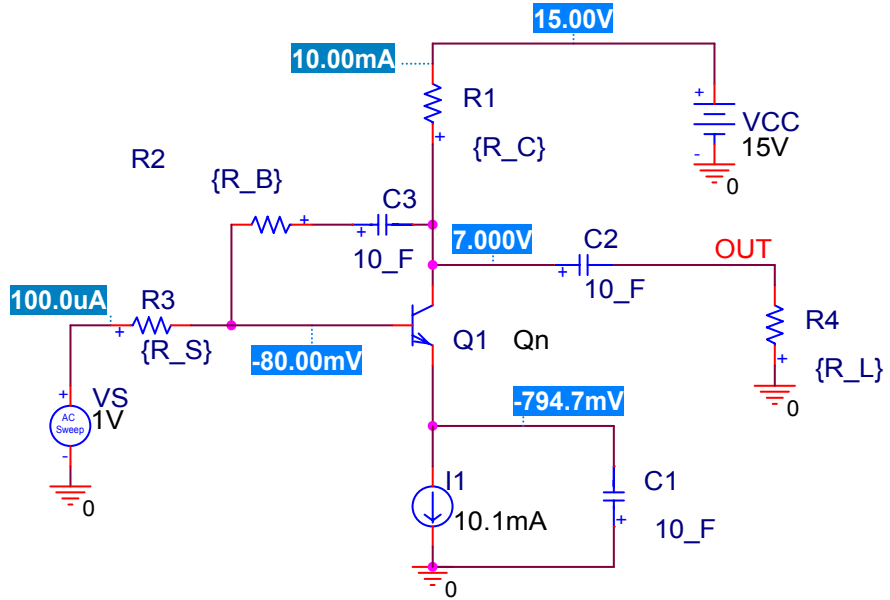

`.model Qn NPN (Is={I_S} Bf={B_F} Cjc={C_JC} Cje={C_JE} Tf={T_F})`

FIGURE 4

Common emitter amplifier

Select the value of resistor R_B to obtain a bandwidth of 6 MHz. Assume $V_{TH} = 25.864\text{ mV}$. Note that the transistor has infinite Early voltage.

Problem 4: Stability

Follow the outline procedure at the top of the exam with headings for each major step in the solution. **No points for answer without an outline of the solution.**
A mish-mash of calculations is not an acceptable outline.

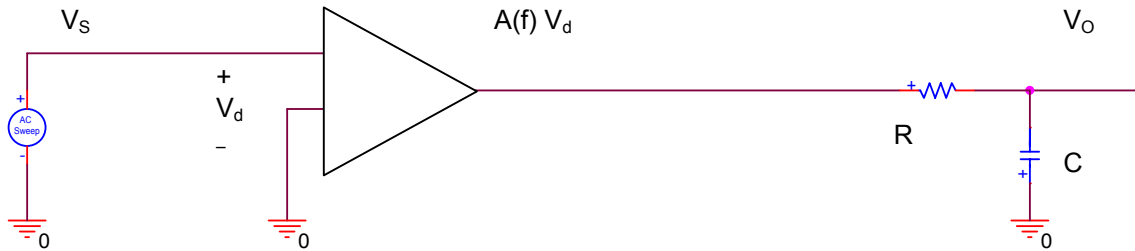


FIGURE 5 Open-loop amplifier; the op amp has infinite input resistance and zero output resistance

The amplifier of Figure 5 contains an RC-network to adjust its frequency response. For the amplifier of Figure 5, select C to make a feedback voltage amplifier using this open-loop amplifier exhibit a 30° phase margin when β_{FB} has a value of $1/\beta_{FB} = 30$ dB. Use Bode plots to do your design. Assume the op amp has a gain function given by

EQ. 1

$$A(f) = \frac{A_0}{\left(1 + j \frac{f}{f_1}\right) \left(1 + j \frac{f}{f_2}\right) \left(1 + j \frac{f}{f_3}\right)},$$

with $A_0 = 10^5 \text{V/V}$, $f_1 = 10^5 \text{Hz}$, $f_2 = 10^6 \text{Hz}$, and $f_3 = 10^7 \text{Hz}$, and assume that the value of $R = 10 \text{M}\Omega$. The op amp has infinite input resistance and zero output resistance