

ECE 304: Final Exam Fall 2000

1. Short questions to be answered in words and diagrams (not equations):
 - 1.1 List the advantages and disadvantages of feedback
 - 1.2 What are the classifications of output amplifiers, what do they mean, and what are the advantages and disadvantages of each?
 - 1.3 What are the advantages and disadvantages of a bypass capacitor?
 - 1.4 What is a cascode circuit? Sketch one that uses bipolar transistors, and explain its advantages in words.
 - 1.5 What is an active load, and what is its advantage over a resistor as load in a common source amplifier?
 - 1.6 Sketch a MOSFET differential amplifier circuit using an active load.
 - 1.7 What is a current mirror, and what is its advantage in a differential amplifier?
 - 1.8 Sketch a circuit for a p-channel MOSFET current mirror.
 - 1.9 For a transconductance amplifier, which type of feedback connection should be used in the input and which in the output? Explain your reasoning.
 - 1.10 Would you model a transresistance amplifier as a Norton source or as a Thevenin source? Explain your answer.
 - 1.11 Would you drive a transconductance amplifier with a Norton source or with a Thevenin source? Explain your answer.
 - 1.12 Why would you use an emitter follower as an input stage?
 - 1.13 Why would you use an emitter follower as an output stage?
 - 1.14 What does the "mid-band region" of an amplifier mean?
 - 1.15 What is the Miller effect? The Miller approximation?
 - 1.16 What are the four types of amplifier considered in feedback theory? Imagine a two-port representation of the amplifier's feedback network. For each type of amplifier, specify the dependent source (e.g., VCVS, CCCS, etc.) that provides the feedback signal. Explain your answers.
 - 1.17 Sketch the circuit for a V_{BE} -multiplier power amplifier. Explain how the multiplier controls output waveform distortion, and why it is called a V_{BE} -multiplier.
 - 1.18 Using a circuit diagram, explain the current flow patterns at the conditions of maximum and of minimum output voltage for the V_{BE} -multiplier power amplifier.

2. For the amplifier in Fig. 1.

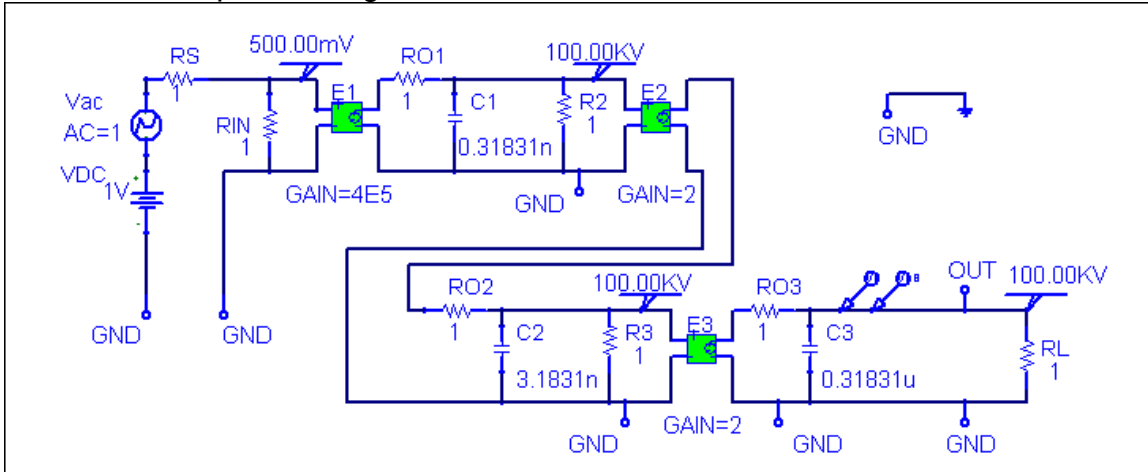


FIGURE 1: BLOCK DIAGRAM OF THREE-STAGE AMPLIFIER. TO ALLOW A CHECK ON YOUR WORK, THE DC VOLTAGES (ZERO FREQUENCY) ARE SHOWN AT SEVERAL POINTS USING Viewpoints.

- 2.1 Calculate the pole frequencies **in Hertz**. For numerical convenience, capacitor values all are proportional to $1/\pi$ and resistor values all are 1Ω .
 - 2.2 Sketch the Bode phase and gain diagrams for V_{OUT}/V_{ac} . Label all slopes and break frequencies. The x-axis should be Hertz, not radians.
 - 2.3 Determine the gain and phase margins when this amplifier is used for a feedback amplifier with feedback $\beta_{FB} = 10^{-2}V/V$
 - 2.4 Add a pole to the open loop amplifier to realize a phase margin of 45° for feedback $\beta_{FB} = 10^{-2}V/V$. Sketch the Bode phase and gain plots of the compensated amplifier. Specify the frequency of the added pole, all slopes and break frequencies.
 - 2.5 Indicate how your diagrams can be used to determine the gain and phase margins for the compensated amplifier and give their values.
3. With the amplifier circuit in Fig. 2,
 - 3.1 Sketch a small-signal circuit valid at high frequencies.
 - 3.2 Decide what limits the corner frequency. Is it the Miller effect? Why or why not?
 - 3.3 Draw another high-frequency equivalent circuit like that above (Question 3.1), but simplified to apply for frequencies in the vicinity of the high-frequency corner. Simplify by leaving out unimportant elements based upon the Q-point values of Table 1 below, and by using your knowledge of how the circuit works. Justify your simplifications in words.

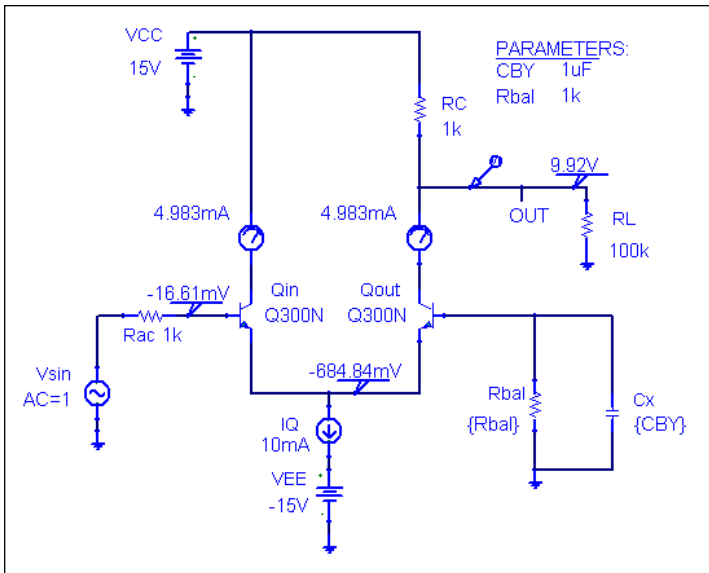


FIGURE 2: AMPLIFIER CIRCUIT FOR PROBLEM 3.

3.4 Generate a high-frequency block equivalent like that shown in Fig. 3 and provide formulas for all circuit components and the gain. To avoid a huge mess, take advantage of any approximations suggested by the Q-point data in Table 1, and also use your knowledge of which capacitors are likely to determine the corner frequency.

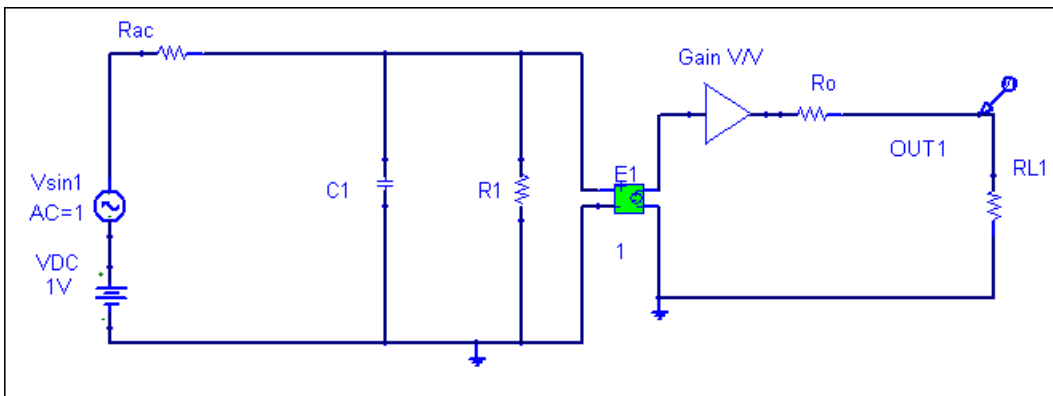


FIGURE 3: BLOCK DIAGRAM FOR HIGH-FREQUENCY EQUIVALENT CIRCUIT OF FIG. 2.

3.5 Evaluate the components and the gain for Fig. 3 using the Q-point data below.

TABLE 1: Q-POINT DATA FOR TRANSISTORS IN FIG. 1.

NAME	Q_Qin	Q_Qout
MODEL	Q300N	Q300N
IB	1.66E-05	1.66E-05
IC	4.98E-03	4.98E-03
VBE	6.68E-01	6.68E-01
VBC	-1.50E+01	-9.93E+00
VCE	1.57E+01	1.06E+01
BETADC	3.00E+02	3.00E+02
GM	1.93E-01	1.93E-01
RPI	1.56E+03	1.56E+03
RX	0.00E+00	0.00E+00
RO	1.00E+12	1.00E+12
CBE	4.74E-11	4.74E-11
CBC	1.10E-12	1.25E-12
CJS	0.00E+00	0.00E+00
BETAAC	3.00E+02	3.00E+02
CBX	0.00E+00	0.00E+00
FT	6.32E+08	6.30E+08

- 3.6 Using Fig. 3, find a formula for the corner frequency in terms of C_1 , R_1 , etc.
- 3.7 Evaluate your formula for the corner frequency. A Bode gain plot is shown below to check your results.

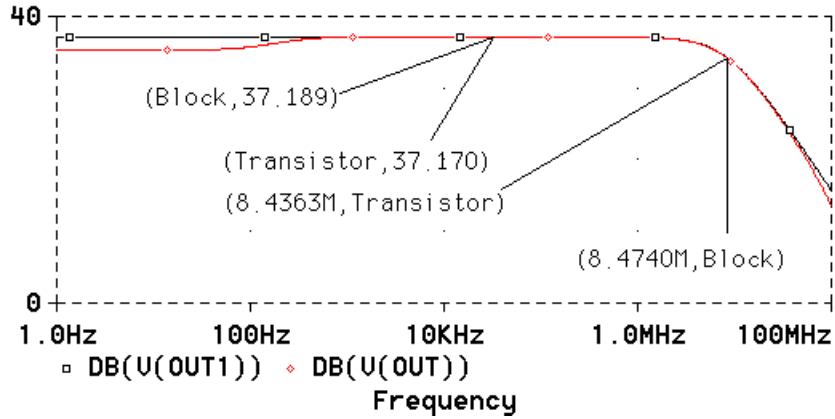


Figure 4: Bode gain plots showing the corner frequency of Fig. 2 (Transistor) and of Fig. 3 (Block diagram).