

ECE 304: Final Exam Fall '01

PROBLEM 1 (25 POINTS)

1. Define *gain margin* and *phase margin* using Bode plots for a three-pole amplifier as an example.
2. State the *rate-of-closure rule* and illustrate with a Bode plot.
3. Using a Bode gain plot, identify the *midband* region of an amplifier. Indicate in what regions you would use the *short-circuit time constant method* and the *open-circuit time constant method* to find the corner frequencies. Write a formula for each region expressing the corner frequencies as a function of the time constants.
4. Describe a situation where using a voltage follower could increase the bandwidth of an amplifier. Sketch the circuit.
5. Sketch the circuit for a *cascode* amplifier. Explain its advantages and how they are achieved.

PROBLEM 2 (25 POINTS)

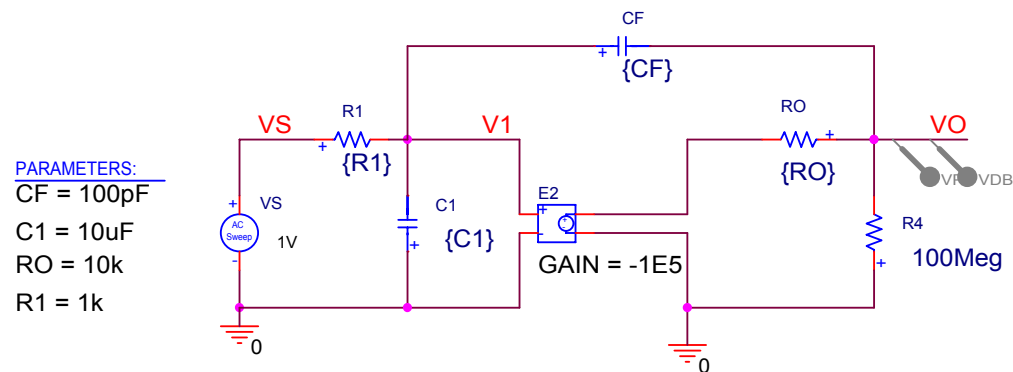


FIGURE 1:

Macromodel of two-pole amplifier using the VCVS PSPICE part E; gain is -10^5V/V .

For the double-pole amplifier of Figure 1,

- Derive a formula for the exact (no approximations) frequency dependence of the gain, V_O/V_S . Treat R_4 as infinite.
- Derive approximate formulas for the two pole frequencies assuming wide separation.
- Using the given parameter values, make a Bode phase and Bode dB gain plot vs. frequency in Hz over the range $1\text{Hz} \leq f \leq 100\text{MHz}$. Mark values and frequencies for each break point and mark slopes/decade of frequency.
- Define the Miller approximation and discuss its validity for the corner frequency of this example.

PROBLEM 3 (25 POINTS)

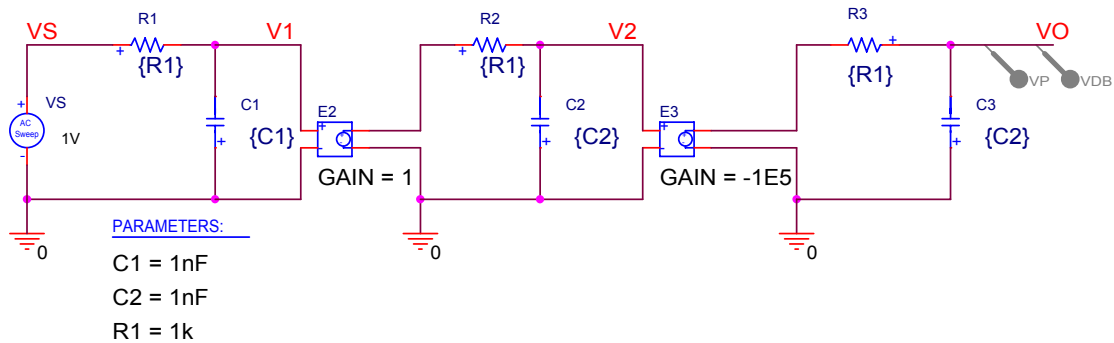


FIGURE 2:

Macromodel of triple-pole amplifier using two VCVS PSPICE parts E; first-stage gain is 1V/V ; second-stage gain is -10^5V/V .

For the triple-pole amplifier of Figure 2,

- Draw the open-loop Bode plots. Label all corners and slopes.
- Move one pole to obtain zero phase margin if the amplifier is used in a non-inverting amplifier with feedback $\beta=1\text{ V/V}$. Use Bode plots for a first guess and use formulas to make any needed adjustments.
- Draw the open-loop Bode plots with the new pole for frequencies from 1 mHz to the unity loop-gain frequency f_1 . Label all corners and slopes.
- Find the value of capacitance C_1 that will result in the new pole frequency.

PROBLEM 4 (35 POINTS)

Parts for Problem 1 are shown in Figure 3. They are to be connected to form a feedback amplifier that provides a specified AC current to the load resistor R_L .

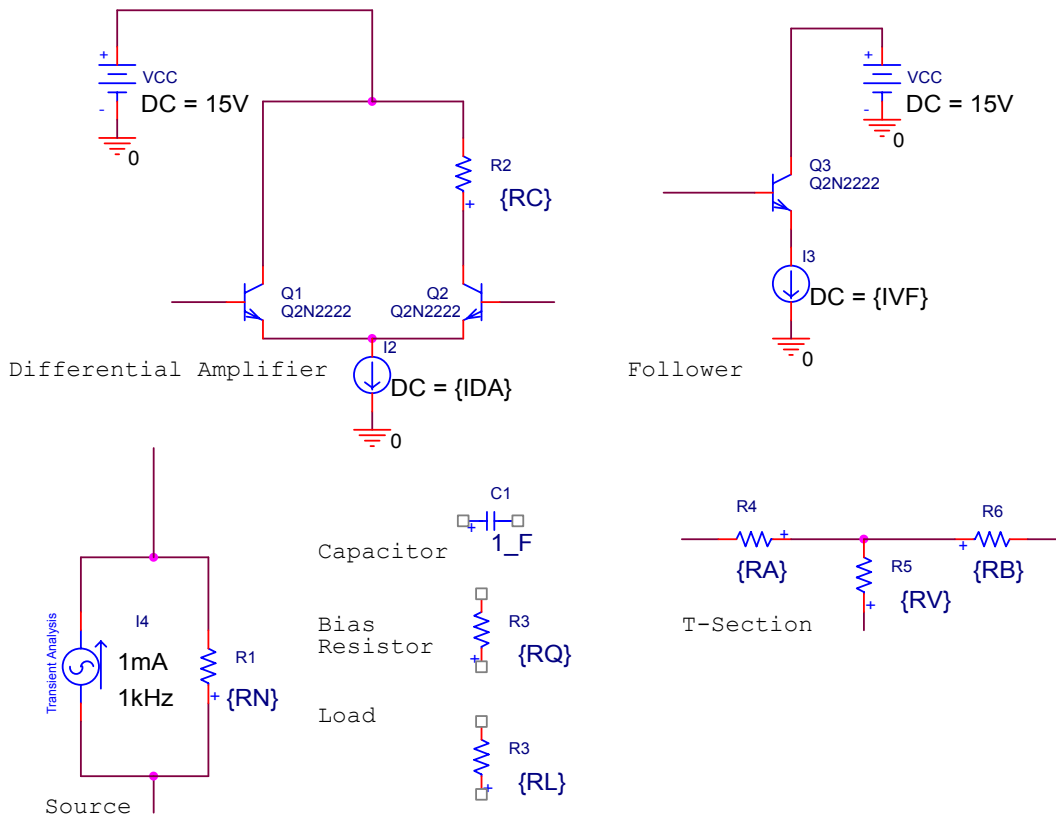


FIGURE 3:

Parts available are one each of diff amp, follower, source, load, bias resistor, capacitor, and T-section

Given only the parts shown in Figure 3, make a schematic showing how to connect them to provide a specified current into load R_L . The following specifications are given:

1. $R_L = 100\Omega$, $R_N = 1\text{ k}\Omega$
2. AC load current is 20 mA amplitude with no clipping for 1 mA AC input
3. Diff amp to have maximum difference-mode gain consistent with specifications 1 & 2.
4. Voltage follower to have minimum DC bias current consistent with specifications 1 & 2
5. T-section resistor values should be determined. Zero values are OK if desirable.

Marks are based on your detailed answers to the following questions. Your design calculations should be keyed to these questions so I can locate where and how you executed your decisions.

Explain the following parts of your design choices in words:

1. How did you select the type of feedback?
2. How did you determine the T-section resistor values (R_A , R_B , R_V)?
3. How did you decide the follower DC bias current (I_{VF})?
4. How did you decide the diff amp DC bias current (I_{DA})?
5. How did you determine the value of R_C ?
6. Explain your use (or not) of the coupling capacitor C_1 .
7. Explain your use (or not) and sizing of the bias resistor R_Q .

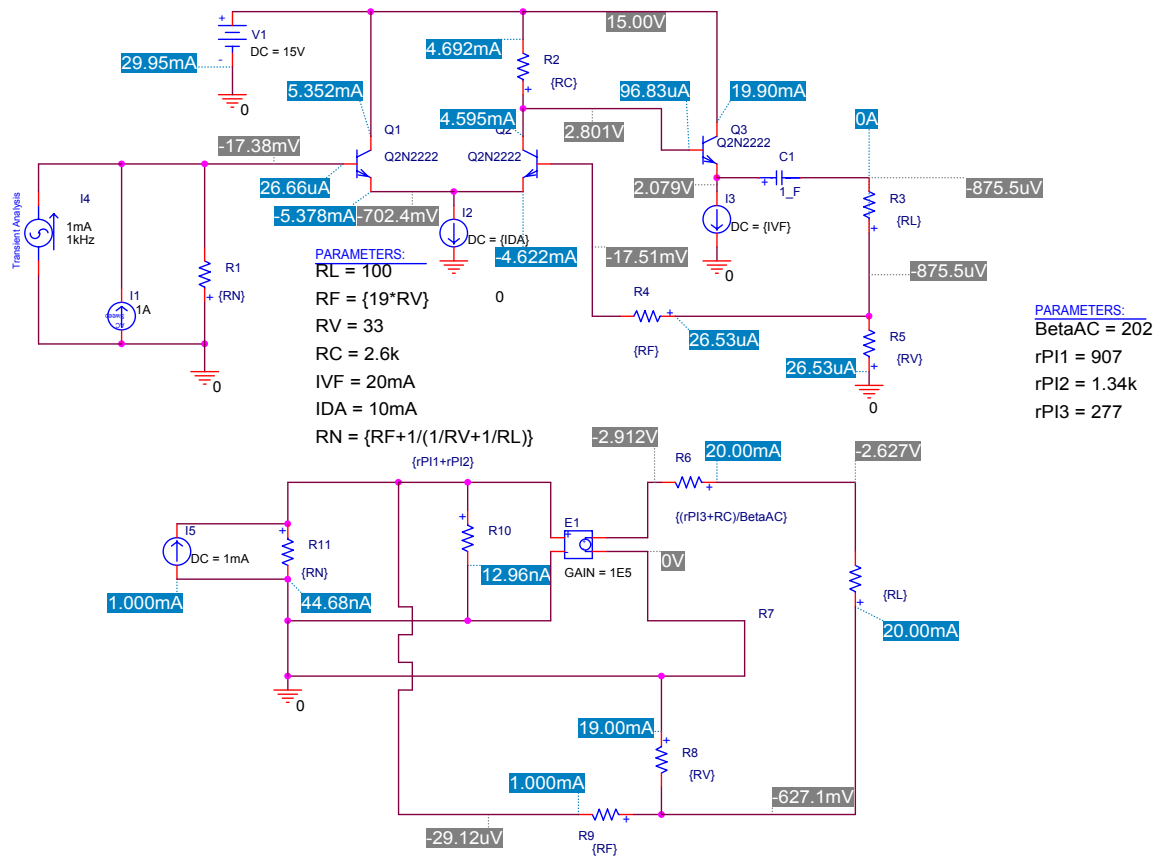


FIGURE 4:
 Solution for last problem

