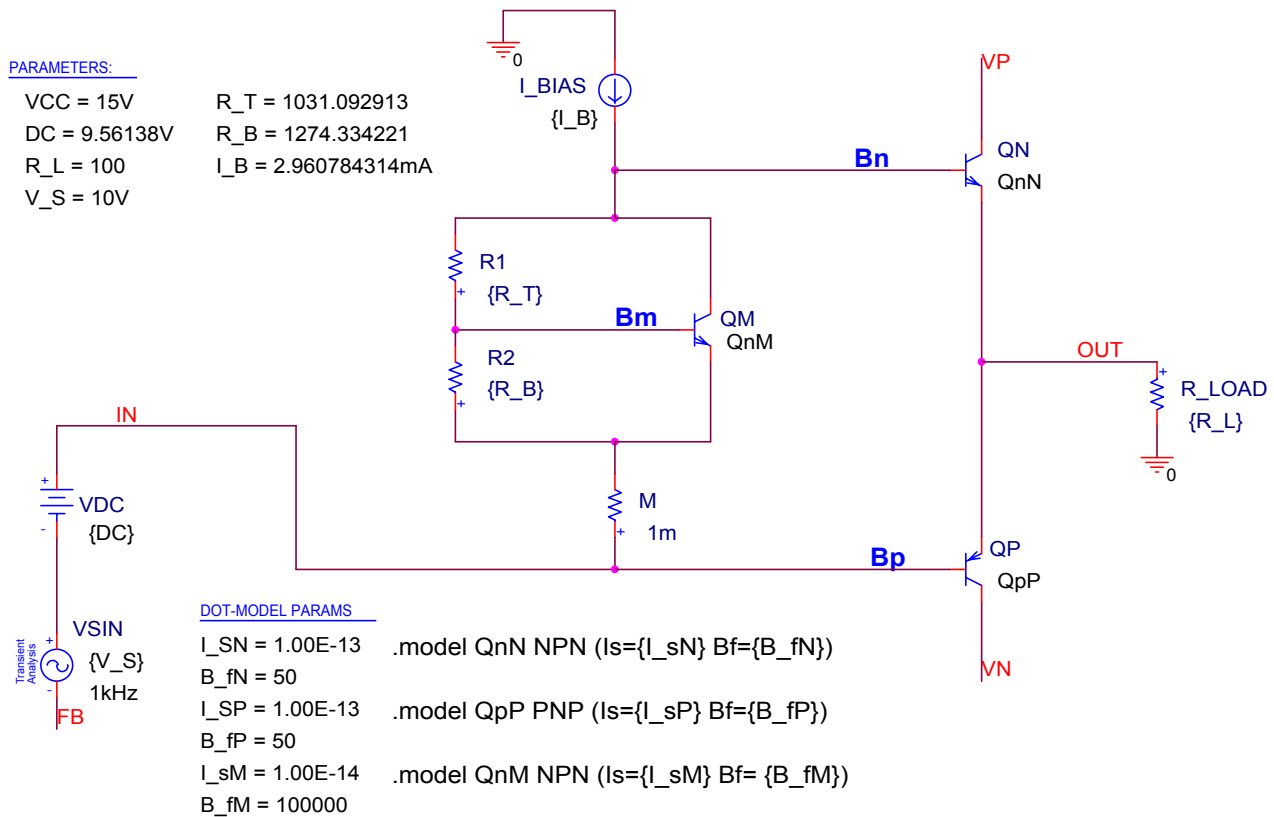


# ECE 304: Design of Simplified $V_{BE}$ -Multiplier Output Stage

## Schematic



**FIGURE 1**  
 A simplified  $V_{BE}$ -multiplier output stage

In the schematic of Figure 1, the  $1\text{m}\Omega$  resistor M is simply a PSpice convenience used to get PSpice to monitor the current in the multiplier and label it on the schematic. It doesn't affect the circuit operation, and is not really part of the circuit. The multiplier can use a PNP or an NPN transistor.

### Objectives

We will design this stage using this input information: value of load  $R_L$ , desired output swing  $V_O$ , and desired harmonic distortion.

### Simplifications

We use a current source for biasing the stage: in practice this would be a current mirror. The main differences are that the mirror cannot be driven too high or it will saturate, and the mirror has a current that varies with the voltage drop across it. We also assume the  $\beta$ -value for the multiplier is very large, so the multiplier base current doesn't matter.

### Design variables

Design variables are variables we introduce to simplify the design or to make it easier to understand. They often are not actual circuit component values, like resistor values, although sometimes they are.

One design variable is the Q-point emitter current of transistor  $Q_N$  for  $V_{OUT} = 0\text{V}$ , namely  $I_Q$ . This current is a measure of the crossover distortion, with a larger  $I_Q$  implying less crossover distortion. We do not have a simple connection between  $I_Q$  and the specified distortion, so we use  $I_Q$  in the design and then adjust  $I_Q$  using PSpice to get the crossover distortion we want.

Two other design variables are used, which are related to how we think the circuit works. They are the minimum multiplier current  $I_M$  (the smallest current flowing through resistor M), and the smallest collector current flowing through the multiplier transistor  $I_{C_{MIN}}$ . The idea behind these two variables is that the multiplier should not be allowed to cut off. Therefore, we need to set the minimum current  $I_{C_{MIN}}$  large enough to avoid cutoff. When this current  $I_{C_{MIN}}$  flows in the multiplier transistor, the current in the multiplier is larger than  $I_{C_{MIN}}$  because of the current in the resistor divider made up of  $R_T$  and  $R_B$ . We set the minimum multiplier current at  $I_M$  to avoid starving the base current of the multiplier transistor. These two currents are not known in advance, so they are adjustable parameters of the design that can be tweaked to obtain good performance.

Among other things, we want to insure that the gain of the stage is nearly one for the entire range of output voltages, and that involves (i) keeping the resistance of the multiplier low, and (ii) keeping the stage linear, which is hardest to achieve for large voltages. The harmonic distortion will be caused by a combination of crossover distortion and the distortion due to this nonlinearity. For the moment, we imagine that the choice of  $I_{C_{MIN}}$  and  $I_M$  might affect these two performance characteristics. As with  $I_Q$ , we will find from PSPICE just what their effects are.

### Analysis

The analysis is based on two bias conditions, the high output voltage condition when  $v_{OUT} = V_O$ , the maximum output swing, and the Q-point where the output voltage  $v_O = 0V$ . Each condition allows part of the design to be found.

#### High output voltage

This bias condition tells us the correct values for  $I_B$  and  $R_B$ .

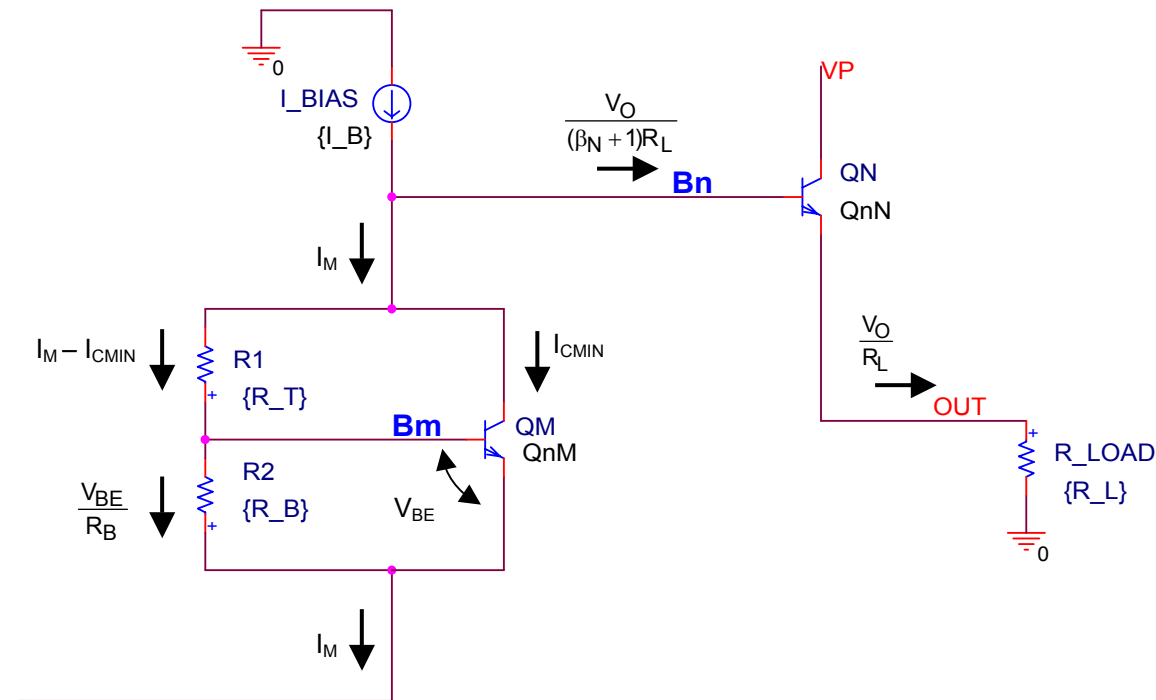


FIGURE 2

High output voltage case with output voltage  $v_O = V_O$ , the maximum output voltage  
 In the high output voltage case, the PNP is cutoff, so the circuit is as Figure 2. KCL at the base node of QN determines the bias current  $I_B$ :

EQ. 1

$$I_B = I_M + \frac{V_O}{(\beta_N + 1)R_L}$$

The diode law determines  $V_{BE}$ :



We design the multiplier to produce the voltage  $V_{BB}$  of EQ. 4. This voltage is set by the sum of the voltage drops across the resistors  $R_T$  and  $R_B$ . The drop across  $R_B$  is the base-emitter voltage  $V_{BEQ}$  of the multiplier transistor. We have to find this voltage. We begin with the diode law, which gives the base-emitter voltage in the multiplier as:

**EQ. 6**

$$V_{BEQ} = V_{TH} \ln(I_C / I_{SM}).$$

To use EQ. 6, we need the collector current  $I_C$ . To find  $I_C$ , we find the current in the resistor branch and apply KCL to the node at the top of the multiplier. First, Ohm's law and  $V_{BEQ}$  determine the current in  $R_B$  as:

**EQ. 7**

$$I_{RB} = V_{BEQ} / R_B.$$

Neglecting base current to the multiplier transistor,  $I_{RB} \approx I_{RT}$ . We then know the current  $I_C$  in the multiplier transistor using KCL at the collector:

**EQ. 8**

$$I_C = I_B - \frac{I_Q}{\beta_N + 1} - I_{RT} \approx I_B - \frac{I_Q}{\beta_N + 1} - \frac{V_{BE}}{R_B}.$$

We plug EQ. 8 into EQ. 6 to find  $V_{BEQ}$ :

**EQ. 9**

$$V_{BEQ} = V_{TH} \ln \left( \frac{I_B - I_Q / (\beta_N + 1) - V_{BEQ} / R_B}{I_{SM}} \right).$$

EQ. 9 is solved by iteration beginning with substitution on the right side using  $V_{BEQ} \approx 0.7$  V, evaluating EQ. 9 for a new  $V_{BEQ}$ , substituting the new value on the right, and so forth. We now know  $V_{BEQ}$ , and the current  $I_{RB} = V_{BEQ} / R_B \approx I_{RT}$ . The total drop across the multiplier is

**EQ. 10**

$$V_{BB} = I_{RT} R_T + I_{RB} R_B \approx (R_T + R_B) V_{BEQ} / R_B = (1 + R_T / R_B) V_{BEQ}.$$

EQ. 10 is the reason the circuit is called the  $V_{BE}$ -multiplier, namely, the voltage drop across it multiplies  $V_{BE}$  by the factor  $(1 + R_T / R_B)$ . Using the known value of  $V_{BB}$  from EQ. 4 in EQ. 10, we find the necessary value of  $R_T$  as shown in EQ. 11 below

**EQ. 11**

$$R_T = \left( \frac{V_{BB}}{V_{BEQ}} - 1 \right) R_B.$$

The design is now complete, with  $R_T$  from EQ. 11,  $R_B$  from EQ. 3, and  $I_B$  from EQ. 1.

## Summary

The input data includes the dot-model parameters of the transistors, the maximum output swing voltage  $V_O$ , the minimum load resistance  $R_L$ , and the maximum allowed harmonic distortion.

The design is based upon three design variables, the Q-point current  $I_Q$  in the output transistors at zero output voltage, the minimum multiplier current  $I_M$ , and the minimum multiplier transistor's collector current  $I_{CMIN}$ .

Current  $I_Q$  controls distortion due to crossover, which can be estimated using Fourier analysis of a TRANSIENT simulation profile in PSpice.

The two minimum currents  $I_M$  and  $I_{CM}$  flow in the *high* voltage output case, because it is in the high voltage case that the base current to the output transistor is high. They are specified to avoid cutoff of the multiplier transistor in this worst-case situation, and have some influence on the amplifier gain and linearity.

## PSpice verification of analysis

### Spreadsheet

	D	E	F	G	H	I	J
				=VBE_min/(I_M-I_Cmin)			
3		<b>VBE Multiplier Output Stage</b>					
4		<b>Charts Worksheet</b>					
5			<b>Input Data Here</b>			<b>Design Summary</b>	
6		Minimum multiplier current	I_M(mA)=	1		<b>Don't Touch</b>	
7		Minimum multiplier IC	I_Cmin(mA)=	0.5			
8		Load resistor	R_L=	100		R_T=	1031.09291
9		Thermal voltage	VTH=	0.025864		R_B=	1274.33422
10		Multiplier scale current	IsM=	1.00E-14		I_B(mA)=	2.96078431
11		PNP scale current	IsP=	1.00E-13			
12		NPN scale current	IsN=	1.00E-13			
13		Multiplier beta	BfM=	100000		<b>Copy to PSpice</b>	
14		PNP beta	BfP=	50			
15		NPN beta	BfN=	50			
16							
17			<b>Specs</b>				
18		Q-point emitter current	I_Q=	2.00E-03			
19		Maximum load voltage	V_Q=	10			
20							
21			<b>Calculated</b>				
22		Minimum multiplier current (A)	I_M=	0.001			
23		Minimum multiplier IC (A)	I_Cmin=	0.0005			
24		Minimum multiplier VBE	VBE_min=	0.637167111			
25		Q-point base-to-base voltage	VBB=	1.225911984			
26		Max NPN VBE	VBE_MAX=	0.714136555			
27		Q-point PNP VBE	VBE_P=	0.612955992			
28		Q-point NPN VBE	VBE_N=	0.612955992			
29		Bias current	I_B=	0.002960784			
30		Bottom multiplier resistor	R_B=	1274.334221			
31		Top multiplier resistor	R_T=	1031.092913			
32							
33			<b>Iteration for Q-point multiplier VBE</b>				
34		First guess multiplier VBE	V_BEQ1=	0.7			
35		Second guess	V_BEQ2=	0.677437131			
36		Third guess	V_BEQ3=	0.677629452			
37		Fourth guess	V_BEQ4=	0.677627819			
38		Final VBEQ	VBE_Q=	0.677627833			

FIGURE 4 Spreadsheet implementing the analysis above

Figure 1 shows a straightforward implementation of the analysis on a spreadsheet

### PSpice evaluation

We look at the two bias conditions used in the analysis, zero output voltage and high output voltage.

ZERO OUTPUT VOLTAGE

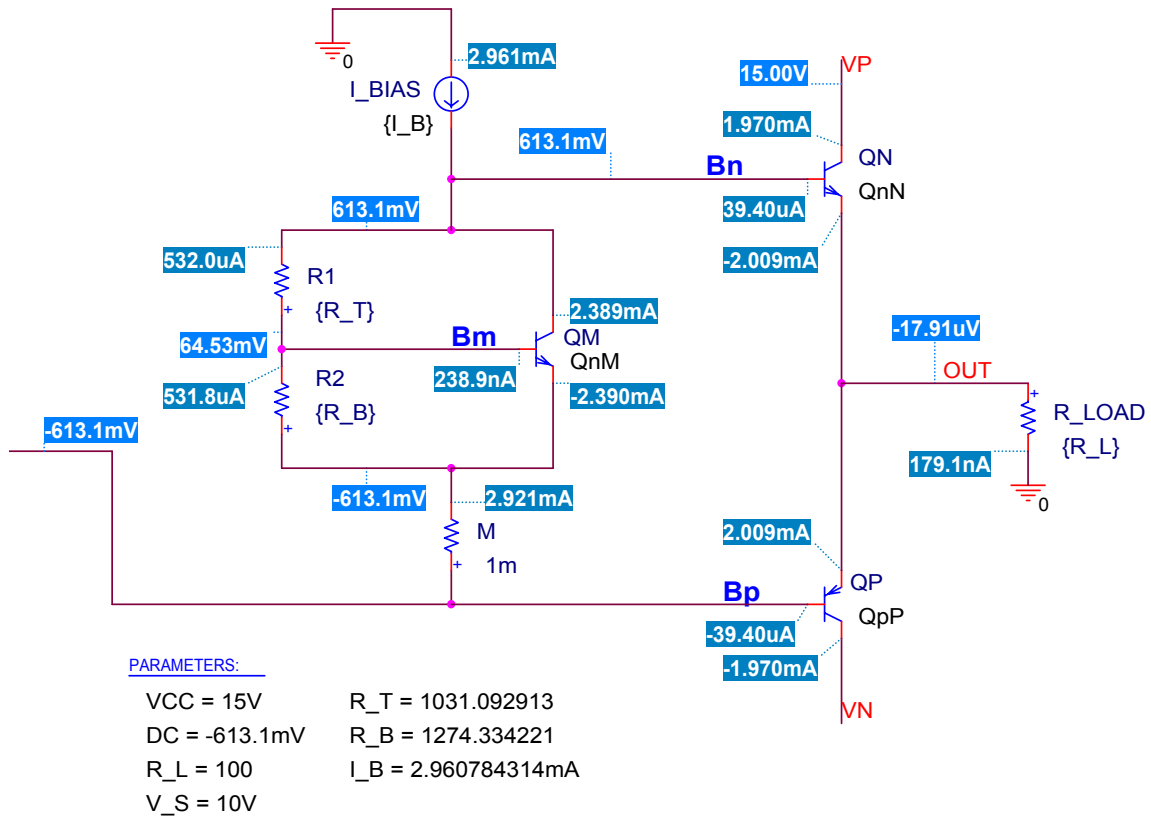


FIGURE 5  
Zero-output case;  $I_Q$  agrees with spreadsheet

 


FIGURE 6  
PSpice values for  $V_{BE}$  and  $V_{BB}$  at the zero-output case; results agree with spreadsheet

Figure 5 and Figure 6 show the spreadsheet agrees with PSpice at zero volts output. The values of  $I_Q$ ,  $V_{BB}$  and  $V_{BE}$  agree with the spreadsheet.

## HIGH OUTPUT VOLTAGE

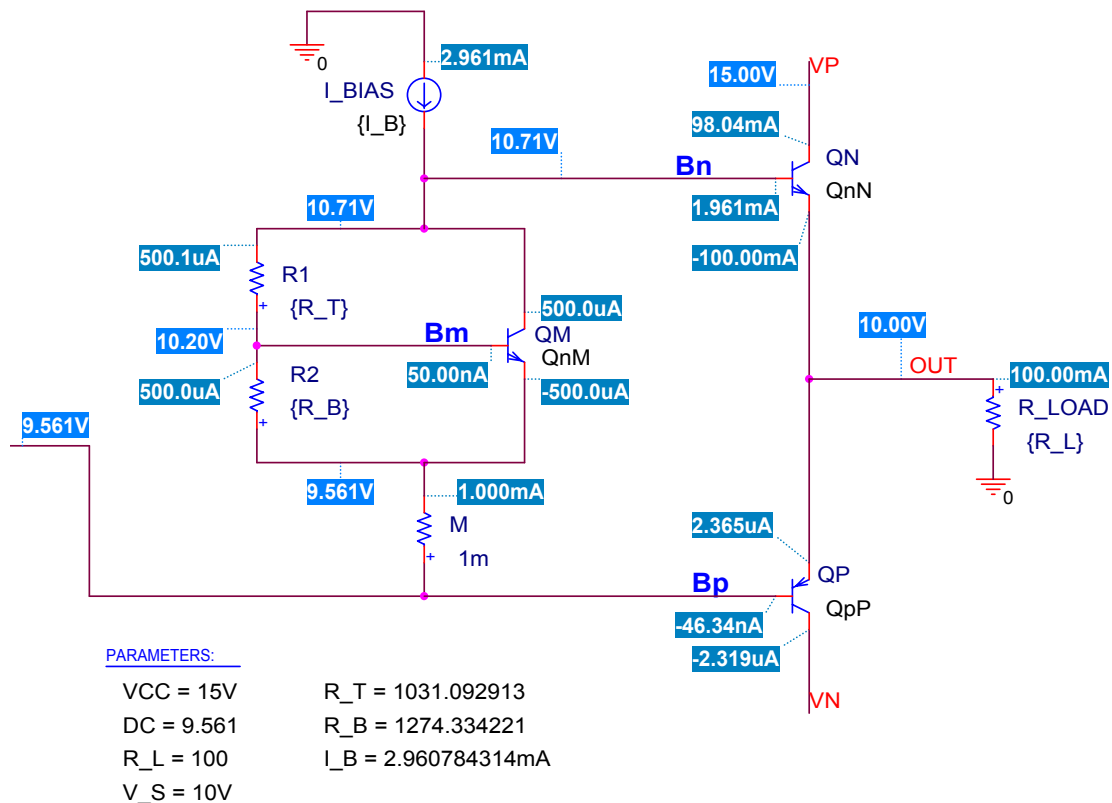


FIGURE 7

High voltage output case  $v_O = 10V$ ; PSpice currents in multiplier agree with spreadsheet;

 


FIGURE 8

PSpice value multiplier  $V_{BE}$  ( $V_{BE\_min}$ ) at the maximum-output case; result agrees with spreadsheet;  $V_{BB}$  at high output is not calculated explicitly on the spreadsheet


Figure 7 and Figure 8 show PSpice agrees with the spreadsheet at  $v_O = 10V$ . Although a current of  $2.4 \mu A$  in  $Q_p$  is not really cut off, it is far too low compared to the current in  $Q_n$  to affect the analysis, so it might as well be cut off. We conclude that the analysis is correct, within its assumptions.

## Distortion evaluation

Having a design, the next step is to compare it with the specifications. We already see that it comes close to driving the output up to  $10V$  and has the selected value of  $I_Q$  when the output is zero. The next question is whether we actually chose good values for  $I_Q$ ,  $I_M$  and  $I_{C_{MIN}}$ .

We do a transient analysis and a gain plot to look at the distortion. If we have an actual number for the harmonic distortion we want, from these plots we can assess whether the amplifier has low enough distortion. If it does not, we can try adjusting  $I_Q$ ,  $I_M$  and  $I_{C_{MIN}}$  to get the best results possible. We may find we have a trade-off situation, where improving one performance goal makes another one worse. If we cannot get the results we want, we will have to use a different circuit.

For sure we will have the trade-off of lower power efficiency for better crossover distortion, as this trade-off is built into the Class AB amplifier.

 


**FIGURE 9**  
Transient output for 10V sinusoidal input

Figure 9 shows we have a pretty good sinusoidal output, although there is some asymmetry because the upswing and downswing aren't quite the same (nonlinearity). A more quantitative estimate of distortion comes from the Fourier analysis feature of PSpice.

HARMONIC NO	FREQUENCY (HZ)	FOURIER COMPONENT	NORMALIZED COMPONENT	PHASE (DEG)	NORMALIZED PHASE (DEG)
1	1.00E+03	9.85E+00	1.00E+00	8.40E-07	0.00E+00
2	2.00E+03	1.63E-02	1.65E-03	9.00E+01	9.00E+01
3	3.00E+03	2.04E-02	2.07E-03	-1.80E+02	-1.80E+02
4	4.00E+03	2.25E-04	2.29E-05	9.00E+01	9.00E+01
5	5.00E+03	1.16E-02	1.17E-03	-1.80E+02	-1.80E+02
6	6.00E+03	8.01E-04	8.13E-05	9.00E+01	9.00E+01
7	7.00E+03	6.37E-03	6.47E-04	-1.80E+02	-1.80E+02
8	8.00E+03	3.19E-04	3.24E-05	9.00E+01	9.00E+01
9	9.00E+03	4.18E-03	4.25E-04	-1.80E+02	-1.80E+02
10	1.00E+04	2.22E-04	2.25E-05	9.00E+01	9.00E+01
11	1.10E+04	2.89E-03	2.93E-04	-1.80E+02	-1.80E+02
12	1.20E+04	1.46E-04	1.48E-05	9.00E+01	9.00E+01
TOTAL HARMONIC DISTORTION =					3.014943E-01 PERCENT

**FIGURE 10**  
PSpice harmonic distortion from PROBE output file is  $\approx 0.3\%$

A very visual idea of the distortion comes from a gain plot, as shown in Figure 11. Figure 11 has a pronounced dip in the center, which is the crossover region. It also sags at high voltages, which is nonlinearity not related to crossover distortion. We see that using lower amplitude, say 8V instead of 10V, will help because the sag at high voltages will not play a part. To get better linearity, maybe we could just design the amplifier for a design  $V_O$  that is larger than the 10V we are really going to use?

 


**FIGURE 11**  
Gain plot for amplifier; crossover distortion results from the dip in the middle of the gain curve; additional distortion is present because of fall-off at large output voltages



We also could look at a few different values of the design parameters  $I_Q$ ,  $I_M$  and  $I_{CMIN}$  to get an idea of just what they do to the distortion.

### Power efficiency evaluation


Using PSpice we can find the power efficiency of the amplifier. In PROBE we run a TRANSIENT simulation profile. Then we use the PSpice function S() to integrate the current-voltage products for the load (useful power), the two power supplies and the current bias.

 

**FIGURE 12**


PSpice integration of  $I$ - $V$  product for the load; average power = 485.2 mW

Figure 12 shows the integrated  $I$ - $V$  product for the load vs. time  $t$ , which is the total power consumed by the load up to time  $t$ . This power is divided by the period of the waveform  $T=1\text{ms}$ , so the average power over one period is the value of this curve at time  $t=1\text{ms}$ .

 


**FIGURE 13**

Integrated  $I$ - $V$  product for the two power supplies: top curve is sum of power for both supplies showing average power of 924.6 mW, bottom curve is the power delivered by the negative power supply alone

 

**FIGURE 14**

Power delivered by current source  $I_B$  showing average power of 1.8 mW

 

**FIGURE 15**  
Power input by signal source of 11.5mW

The power efficiency is then

**EQ. 12**

$$\eta = \frac{\text{Useful power to load}}{\text{Power input}} = \frac{485.2\text{mW}}{1.8\text{mW} + 11.5\text{mW} + 924.6\text{mW}} = 52\%$$

Neither the power contributed by the signal source nor the DC bias source is large enough to affect the power efficiency, at least in this case.

### Exercises

1. Extend the analysis to include the base current of the multiplier transistor.
2. Extend the analysis to include the Early voltage of the multiplier.
3. Extend the analysis to include different values for  $\beta$  at different current levels; for example,  $\beta_N$  of the NPN is different for high currents than for low currents.
4. Extend the analysis to include a current mirror to supply the bias current, and take into account that the mirror supplies a different current at the Q-point than for maximum output voltage. That is, take the mirror resistance into account.
5. Do a small-signal analysis for both a high and low DC output voltage to see how close the gain is to one, to check the distortion due to gain variation, and to see how the resistance of the multiplier circuit affects the gain.
6. Extend the analysis to include a voltage follower input stage. In this case the downswing analysis is necessary to design the voltage follower so it will not cut off.
7. Make a spreadsheet for each of the above extensions.