

# ECE 274 Digital Logic

## RTL Design Method Examples


*Digital Design 5.3*



THE UNIVERSITY OF  
**ARIZONA**  
TUCSON ARIZONA

# Digital Design

## Chapter 5: RTL Design

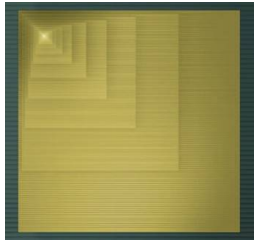

Slides to accompany the textbook *Digital Design*, First Edition,  
by Frank Vahid, John Wiley and Sons Publishers, 2007.  
<http://www.dvahid.com>

Copyright © 2007 Frank Vahid

Instructors of courses requiring Vahid's *Digital Design* textbook (published by John Wiley and Sons) have permission to modify and use these slides for customary course-related activities, subject to keeping this copyright notice in place and unmodified. These slides may be posted as ~~unmodified~~ pdf versions on publicly-accessible course websites. PowerPoint source (or pdf with animations) may ~~not~~ be posted to publicly-accessible websites, but may be posted for students on internal protected sites or distributed directly to students by other electronic means. Instructors may make printouts of the slides available to students for a reasonable photocopying charge, without incurring royalties. Any other use requires explicit permission. Instructors may obtain PowerPoint source or obtain special use permissions from Wiley – see <http://www.dvahid.com> for information.

## RTL Design

*RTL Design Method*

5.2


Step	Description
Step 1 <i>Capture a high-level state machine</i>	Describe the system's desired behavior as a high-level state machine. The state machine consists of states and transitions. The state machine is "high-level" because the transition conditions and the state actions are more than just Boolean operations on bit inputs and outputs.
Step 2 <i>Create a datapath</i>	Create a datapath to carry out the data operations of the high-level state machine.
Step 3 <i>Connect the datapath to a controller</i>	Connect the datapath to a controller block. Connect external Boolean inputs and outputs to the controller block.
Step 4 <i>Derive the controller's FSM</i>	Convert the high-level state machine to a finite-state machine (FSM) for the controller, by replacing data operations with setting and reading of control signals to and from the datapath.

3

## RTL Design

*RTL Example: Video Compression – Sum of Absolute Differences*

Only difference: UFO moving

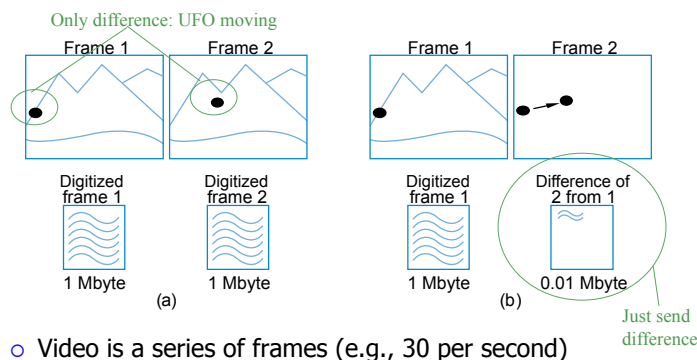


- Video is a series of frames (e.g., 30 per second)
- Most frames similar to previous frame
  - Compression idea: just send difference from previous frame

4
 
## RTL Design

RTL Example: Video Compression – Sum of Absolute Differences




- Need to quickly determine whether two frames are similar enough to just send difference for second frame
  - ▢ Compare corresponding 16x16 "blocks"
    - Treat 16x16 block as 256-byte array
  - ▢ Compute the absolute value of the difference of each array item
  - ▢ Sum those differences – if above a threshold, send complete frame for second frame; if below, can use difference method (using another technique, not described)

5
 
## RTL Design

RTL Example: Video Compression – Sum of Absolute Differences




- Want fast sum-of-absolute-differences (SAD) component
  - ▢ When  $go=1$ , sums the differences of element pairs in arrays  $A$  and  $B$ , outputs that sum

6
 
## RTL Design

RTL Example: Video Compression – Sum of Absolute Differences




- **S0**: wait for go
- **S1**: initialize  $sum$  and  $index$
- **S2**: check if done ( $i \geq 256$ )
- **S3**: add difference to  $sum$ , increment index
- **S4**: done, write to output  $sad\_reg$

7

## RTL Design

RTL Example: Video Compression – Sum of Absolute Differences

- Step 2: Create datapath

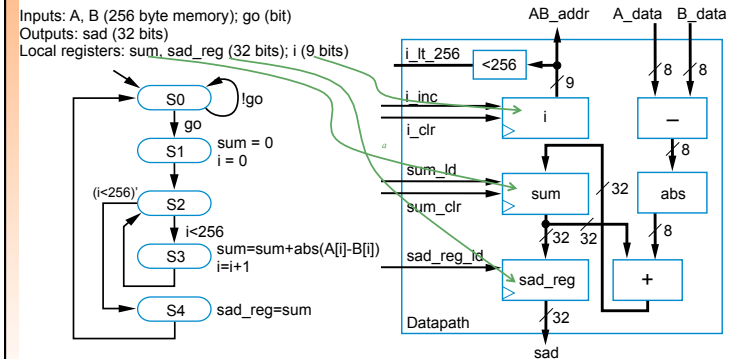


8

## RTL Design
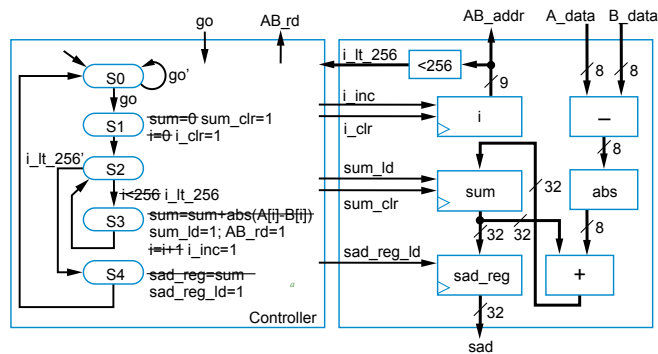
### RTL Example: Video Compression – Sum of Absolute Differences

- Step 3: Connect to controller
- Step 4: Replace high-level state machine by FSM




9

## RTL Design
 
### RTL Example: Video Compression – Sum of Absolute Differences

- Comparing software and custom circuit SAD
  - Circuit: Two states (**S2 & S3**) for each  $i$ ; 256  $i$ 's  $\rightarrow$  512 clock cycles
  - Software: Loop (for  $i = 1$  to 256), but for each  $i$ , must move memory to local registers, subtract, compute absolute value, add to sum, increment  $i$  – say about 6 cycles per array item  $\rightarrow 256 * 6 = 1536$  cycles
  - Circuit is about 3 times (300%) faster
  - Later, we'll see how to build SAD circuit that is even faster





10

## RTL Design

### Pitfalls and Good Practice

- Considering the high-level state machine shown to the right, what is the final value of D in state F?

- 10
- 11
- 12
- 17
- 20

  


11

## RTL Design
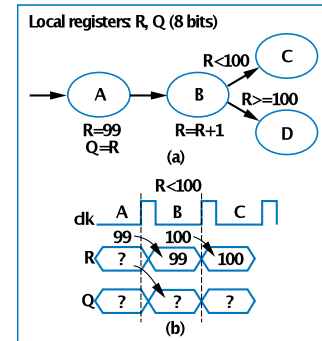
### Pitfalls and Good Practice

- Common pitfall: Assuming register is update in the state it's written
  - All registers updates in each state will happen simultaneously
    - On the next rising clock edge
- Consider the FSM to the right:
  - What is the final value of Q?
  - What is the final state?
  - Answer:
    - Value of Q unknown
    - Final state is C (not D)
  - Why?
    - State A:  $R=99$  and  $Q=R$  happen simultaneously
    - State B:  $R$  not updated with  $R+1$  until next clock cycle, simultaneously with state register being updated





12

## RTL Design Pitfalls and Good Practice

- Considering the high-level state machine shown to the right, what is the final value of D in state F?

- 10
- 11
- 12
- 17
- 20

  


13
 
## RTL Design Pitfalls and Good Practice

- Common pitfall: Reading outputs

- Outputs should only be written
- Solution: Introduce additional register, which can be written and read




14
 
## RTL Design Pitfalls and Good Practice

- Good practice: Register all data outputs

- In fig (a), output  $P$  would show spurious values as addition computes
  - Furthermore, longest register-to-register path, which determines clock period, is not known until that output is connected to another component
- In fig (b), spurious outputs reduced, and longest register-to-register path is clear



15