

ECE 274 Digital Logic

Sequential Logic Design – Sequential Logic Design Process


Digital Design 3.4 – 3.5



Digital Design

Chapter 3: Sequential Logic Design -- Controllers

 Slides to accompany the textbook *Digital Design*, First Edition, by Frank Vahid, John Wiley and Sons Publishers, 2007.
<http://www.dvahid.com>



Copyright © 2007 Frank Vahid

Instructors of courses requiring Vahid's *Digital Design* textbook (published by John Wiley and Sons) have permission to modify and use these slides for customary course-related activities, subject to keeping this copyright notice in place and unmodified. These slides may be posted as ~~unmodified~~ pdf versions on publicly-accessible course websites. PowerPoint source for use with animations may ~~not~~ be posted to publicly-accessible websites, but may be posted for students on internal protected sites or distributed directly to students by other electronic means. Instructors may make printouts of the slides available to students for a reasonable photocopying charge, without incurring royalties. Any other use requires explicit permission. Instructors may obtain PowerPoint source or obtain special use permissions from Wiley – see <http://www.dvahid.com> for information.

Sequential Logic Design Controller Design


Five step controller design process

Step	Description
Step 1 <i>Capture the FSM</i>	Create an FSM that describes the desired behavior of the controller.
Step 2 <i>Create the architecture</i>	Create the standard architecture by using a state register of appropriate width, and combinational logic with inputs being the state register bits and the FSM inputs and outputs being the next state bits and the FSM outputs.
Step 3 <i>Encode the states</i>	Assign a unique binary number to each state. Each binary number representing a state is known as an encoding . Any encoding will do as long as each state has a unique encoding.
Step 4 <i>Create the state table</i>	Create a truth table for the combinational logic such that the logic will generate the correct FSM outputs and next state signals. Ordering the inputs with state bits first makes this truth table describe the state behavior, so the table is a state table.
Step 5 <i>Implement the combinational logic</i>	Implement the combinational logic using any method.

3

Sequential Logic Design Controller Design: Laser Timer Example

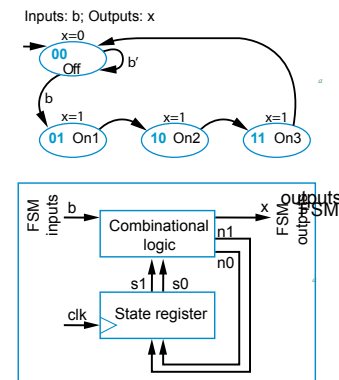- Step 1: Capture the FSM
 - Already done
- Step 2: Create architecture
 - 2-bit state register (for 4 states)
 - Input b, output x
 - Next state signals n1, n0
- Step 3: Encode the states
 - Any encoding with each state unique will work




4

Sequential Logic Design

Controller Design: Laser Timer Example (cont)

- Step 4: Create state table

	Inputs			Outputs		
	s1	s0	b	x	n1	n0
Off	0	0	0	0	0	0
	0	0	1	0	0	1
On1	0	1	0	1	1	0
	0	1	1	1	1	0
On2	1	0	0	1	1	1
	1	0	1	1	1	1
On3	1	1	0	1	0	0
	1	1	1	1	0	0

 


5

Sequential Logic Design

Controller Design: Laser Timer Example (cont)

- Step 5: Implement combinational logic

	Inputs			Outputs		
	s1	s0	b	x	n1	n0
Off	0	0	0	0	0	0
	0	0	1	0	0	1
On1	0	1	0	1	1	0
	0	1	1	1	1	0
On2	1	0	0	1	1	1
	1	0	1	1	1	1
On3	1	1	0	1	0	0
	1	1	1	1	0	0

 

$x = s1 + s0$ (note from the table that $x=1$ if $s1 = 1$ or $s0 = 1$)

$n1 = s1's0b' + s1's0b + s1s0b' + s1s0b$
 $n1 = s1's0 + s1s0$

$n0 = s1's0'b + s1s0'b' + s1s0'b$
 $n0 = s1's0'b + s1s0'$


6

Sequential Logic Design

Controller Design: Laser Timer Example (cont)

- Step 5: Implement combinational logic (cont)

	Inputs			Outputs		
	s1	s0	b	x	n1	n0
Off	0	0	0	0	0	0
	0	0	1	0	0	1
On1	0	1	0	1	1	0
	0	1	1	1	1	0
On2	1	0	0	1	1	1
	1	0	1	1	1	1
On3	1	1	0	1	0	0
	1	1	1	1	0	0

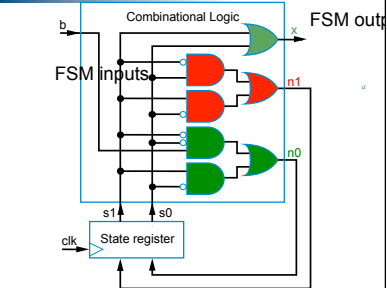


$x = s1 + s0$
 $n1 = s1's0 + s1s0'$
 $n0 = s1's0'b + s1s0'$

7

Sequential Logic Design

Understanding the Controller's Behavior

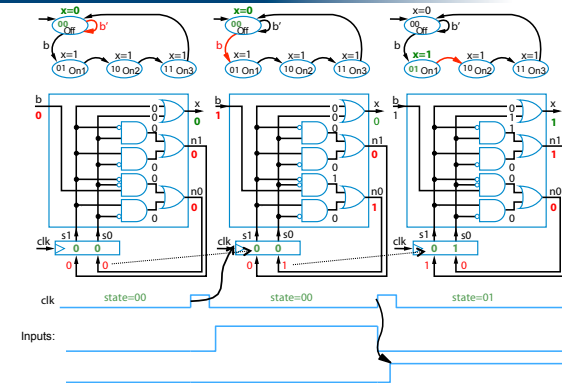


8

Sequential Logic Design

Simplifying Notations


FSMs

 - Assume unassigned output implicitly assigned 0



Sequential circuits

 - Assume unconnected clock inputs connected to same external clock




9

Sequential Logic Design

Controller Example: Secure Car Key

(from earlier example)

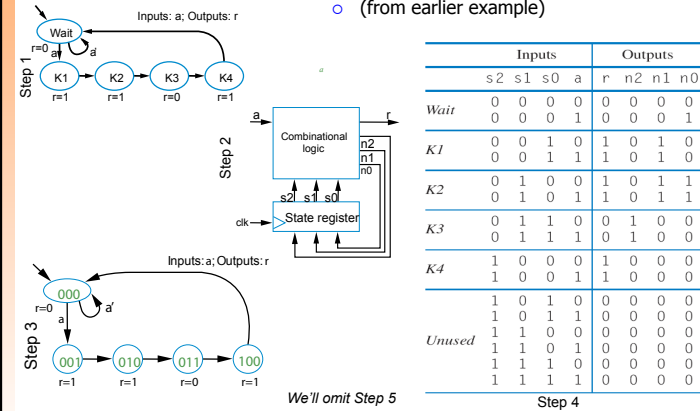



10

Sequential Logic Design

FSM Example: Code Detector

- If we changed the state encoding for the secure car key design to the following, would this affect the final output?


- Yes
- No

  

11

Sequential Logic Design

 In Class Exercise: Button Press Synchronizer




- Want simple sequential circuit that converts button press to single cycle duration, regardless of length of time that button actually pressed
 - We assumed such an ideal button press signal in earlier example, like the button in the laser timer controller

12

Sequential Logic Design

FSM Transitions

 - Is the following FSM valid?
 - Yes
 - No




13

Sequential Logic Design

Common Pitfalls Regarding Transition Properties

- Only one condition should be true
 - For all transitions leaving a state
 - Else, which one?
- One condition must be true
 - For all transitions leaving a state
 - Else, where go?
- Can verify using Boolean algebra
 - Only one condition true: AND of each condition pair (for transitions leaving a state) should equal 0 → proves pair can never simultaneously be true
 - One condition true: OR of all conditions of transitions leaving a state) should equal 1 → proves at least one condition must be true

 

14

Sequential Logic Design

Evidence that Pitfall is Common

- Recall code detector FSM
 - We "fixed" a problem with the transition conditions
 - Do the transitions obey the two required transition properties?
 - Consider transitions of state *Start*, and the "only one true" property


$ar * a'$	$a' * a(r'+b+g)$	$ar * a(r'+b+g)$
$= (a*a')r$	$= (a*a')(r'+b+g)$	$= (a*a)r*(r'+b+g)$
$= 0*r$	$= 0*(r'+b+g)$	$= a*r*(r'+b+g)$
$= 0$	$= 0$	$= ar'r+arb+arg$
		$= 0 + arb+arg$
		$= ar + arg$
		$= ar(b+g)$

Fails! Means that two of *Start*'s transitions could be true

Q: How to solve?

A: ar should be $arb'g'$ (likewise for ab , ag , ar)

 Note: As evidence the pitfall is common, we admit the mistake was not intentional. A reviewer of the book caught it.





Intuitively: press red and blue buttons at same time: conditions ar , and $a(r'+b+g)$ will both be true. Which one should be taken?

15

Sequential Logic Design

Flip-Flop Set and Reset Inputs

  - Some flip-flops have additional inputs
 - Synchronous reset: clears Q to 0 on next clock edge
 - Asynchronous reset: clear Q to 0 immediately (not dependent on clock edge)
 - Example timing diagram shown




16

Sequential Logic Design

Initial State of a Controller

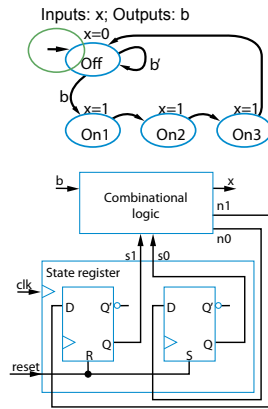- All our FSMs had initial state
 - But our sequential circuit designs did not
 - Can accomplish using flip-flops with reset/set inputs
 - Shown circuit initializes flip-flops to 01
 - Circuits typically have power on reset circuitry to automatically reset circuit on power up




17

Sequential Logic Design

Non-Ideal Flip-Flop Behavior

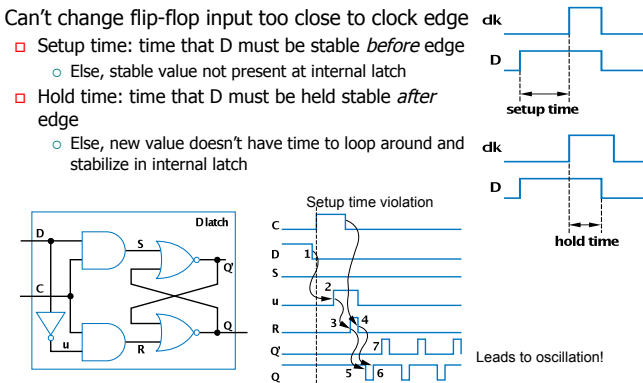- Can't change flip-flop input too close to clock edge
 - Setup time: time that D must be stable *before* edge
 - Else, stable value not present at internal latch
 - Hold time: time that D must be held stable *after* edge
 - Else, new value doesn't have time to loop around and stabilize in internal latch




18

Sequential Logic Design

Metastability

- Violating setup/hold time can lead to bad situation known as **metastable** state
 - Metastable state: Any flip-flop state other than stable 1 or 0
 - Eventually settles to one or other, but we don't know which
 - For internal circuits, we can make sure observe setup time
 - But what if input comes from external (asynchronous) source, e.g., button press?
- Partial solution
 - Insert synchronizer flip-flop for asynchronous input
 - Special flip-flop with very small setup/hold time
 - Doesn't completely prevent metastability

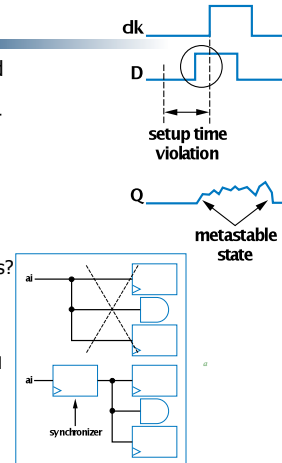


19

Sequential Logic Design

Metastability

- One flip-flop doesn't completely solve problem
- How about adding more synchronizer flip-flops?
 - Helps, but just decreases probability of metastability
- So how solve completely?
 - Can't! May be unsettling to new designers. But we just can't guarantee a design that won't ever be metastable. We can just minimize the mean time between failure (MTBF) -- a number often given along with a circuit

 Probability of flip-flop being metastable is...



20