

ECE 274 Digital Logic – Fall 2008



Sequential Logic Design using Verilog

Verilog for Digital Design Ch. 3




Register Behavior

  - Sequential circuits have storage
- Register: most common storage component
 - N-bit register stores N bits
 - Structure may consist of connected flip-flops



Register Behavior Vectors

 - Typically just describe register behaviorally
 - Declare output Q as reg variable to achieve storage
- Uses vector types
 - Collection of bits
 - More convenient than declaring separate bits like I3, I2, I1, I0
 - Vector's bits are numbered
 - Options: [0:3], [1:4], etc.
 - [3:0]
 - Most-significant bit is on left
 - Assign with binary constant (more on next slide)



```

`timescale 1 ns/1 ns
module Reg4(I, Q, Clk, Rst);
    input [3:0] I;
    output [3:0] Q;
    reg [3:0] Q;
    input Clk, Rst;

    always @(posedge Clk) begin
        if (Rst == 1)
            Q <= 4'b0000;
        else
            Q <= I;
    end
endmodule


module Reg4(I3,I2,I1,I0,Q3,...);
    input I3, I2, I1, I0;
    [I3 I2 I1 I0]
endmodule

module Reg4(I, Q, ...);
    input [3:0] I;
    I: [I3 I2 I1 I0]
    I[3][2][1][0]
endmodule
    
```

v1dd_ch3_Reg4.v

Register Behavior Constants

- Binary constant
 - 4'b0000
 - 4: size, in number of bits
 - b: binary base
 - 0000: binary value
- Other constant bases possible
 - d: decimal base, o: octal base, h: hexadecimal base
 - 12'hFA2
 - h: hexadecimal base
 - 12: 3 hex digits require 12 bits
 - FA2: hex value
 - Size is always in bits, and optional
 - 7hFA2 is OK
 - For decimal constant, size and 'd optional
 - 8'd255 or just 255
 - In previous uses like "A <= 1" 1 and 0 are actually decimal numbers. 'b1 and 'b0 would explicitly represent bits
- Underscores may be inserted into value for readability
 - 12'b1111_1010_0010
 - 8_000_000

 

```

`timescale 1 ns/1 ns
module Reg4(I, Q, Clk, Rst);
    input [3:0] I;
    output [3:0] Q;
    reg [3:0] Q;
    input Clk, Rst;

    always @(posedge Clk) begin
        if (Rst == 1)
            Q <= 4'b0000;
        else
            Q <= I;
    end
endmodule
    
```

v1dd_ch3_Reg4.v

Register Behavior

- Procedure's event control involves Clk input
 - Not the I input. Thus, synchronous
 - "posedge Clk"
 - Event is not just any change on Clk, but specifically change from 0 to 1 (positive edge)
 - negedge also possible
- Process has synchronous reset
 - Resets output Q only on rising edge of Clk
- Process writes output Q
 - Q declared as reg variable, thus *stores* value too

```

timescale 1 ns/1 ns
module Reg4(I, Q, Clk, Rst);
    input [3:0] I;
    output [3:0] Q;
    reg [3:0] Q;
    input Clk, Rst;

    always @(posedge Clk) begin
        if (Rst == 1)
            Q <= 4'b0000;
        else
            Q <= I;
    end
endmodule
    
```

5

Register Behavior Testbench

- reg/wire declarations and module instantiation and module instantiation similar to previous testbenches
- Module uses two procedures
 - One generates 20 ns clock
 - 0 for 10 ns, 1 for 10 ns
 - Note: always procedure repeats
 - Other provides values for inputs Rst and I (i.e., vectors)
 - initial procedure executes just once, does not repeat
 - (more on next slide)

```

timescale 1 ns/1 ns
module Testbench();
    reg [3:0] I_s;
    reg Clk_s, Rst_s;
    wire [3:0] Q_s;

    Reg4 CompToTest(I_s, Q_s, Clk_s, Rst_s);

    // Clock Procedure
    always begin
        Clk_s <= 0;
        #10;
        Clk_s <= 1;
        #10;
    end // Note: Procedure repeats

    // Vector Procedure
    initial begin
        Rst_s <= 1;
        I_s <= 4'b0000;
        @(posedge Clk_s);
        #5 Rst_s <= 0;
        I_s <= 4'b0000;
        @(posedge Clk_s);
        #5 Rst_s <= 0;
        I_s <= 4'b1010;
        @(posedge Clk_s);
        #5 Rst_s <= 0;
        I_s <= 4'b1111;
    end
endmodule
    
```

6

Register Behavior Testbench

- Variables/nets can be shared between procedures
 - Only one procedure should write to variable
 - Variable can be read by many procedures
 - Clock procedure writes to Clk_s
 - Vector procedures reads Clk_s
- Event control "@(posedge Clk_s)"
 - May be prepended to statement to synchronize execution with event occurrence
 - Statement may be just ";" as in example
 - In previous examples, the "statement" was a sequential block (begin-end)
 - Test vectors thus don't include the clock's period hard coded
- Care taken to change input values away from clock edges

```

timescale 1 ns/1 ns
module Testbench();
    reg [3:0] I_s;
    reg Clk_s, Rst_s;
    wire [3:0] Q_s;

    Reg4 CompToTest(I_s, Q_s, Clk_s, Rst_s);


    // Clock Procedure
    always begin
        Clk_s <= 0;
        #10;
        Clk_s <= 1;
        #10;
    end // Note: Procedure repeats

    // Vector Procedure
    initial begin
        Rst_s <= 1;
        I_s <= 4'b0000;
        @(posedge Clk_s);
        #5 Rst_s <= 0;
        I_s <= 4'b0000;
        @(posedge Clk_s);
        #5 Rst_s <= 0;
        I_s <= 4'b1010;
        @(posedge Clk_s);
        #5 Rst_s <= 0;
        I_s <= 4'b1111;
    end
endmodule
    
```

7

Register Behavior Testbench

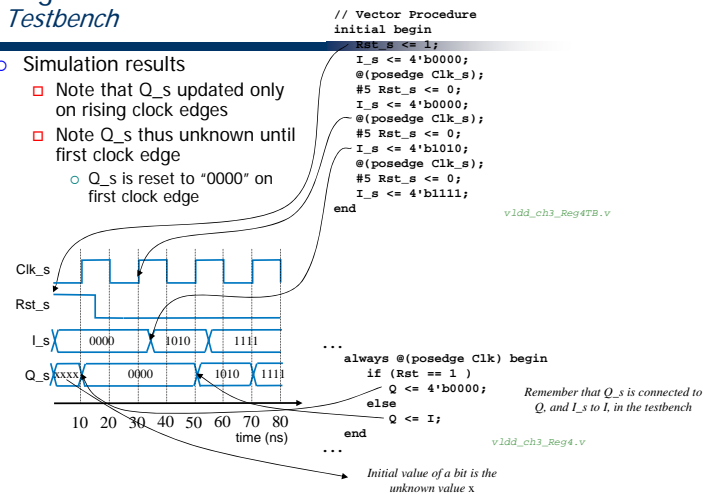- Simulation results
 - Note that Q_s updated only on rising clock edges
 - Note Q_s thus unknown until first clock edge
 - Q_s is reset to "0000" on first clock edge




8

Common Pitfalls

- Using "always" instead of "initial" procedure
 - Causes repeated procedure execution
- Not including any delay control or event control in an always procedure
 - May cause infinite loop in the simulator
 - Simulator executes those statements over and over, never executing statements of another procedure
 - Simulation time can never advance
 - Symptom – Simulator appears to just hang, generating no waveforms

```
// Vector Procedure
always begin
  Rst_s <= 1;
  I_s <= 4'b0000;
  @(posedge Clk_s);
  ...
  @(posedge Clk_s);
  #5 Rst_s <= 0;
  I_s <= 4'b1111;
end

 // Vector Procedure
always begin
  Rst_s <= 1;
  I_s <= 4'b0000;
end
```



9

Common Pitfalls

- Not initializing all module inputs
 - May cause undefined outputs
 - Or simulator may initialize to default value. Switching simulators may cause design to fail.
 - Tip: Immediately initialize all module inputs when first writing procedure

```
// Vector Procedure
always begin
  Rst_s <= 1;
  I_s <= 4'b0000;
  @(posedge Clk_s);
  ...
  @(posedge Clk_s);
  #5 Rst_s <= 0;
  I_s <= 4'b1111;
end
```

10

Common Pitfalls


- Forgetting to explicitly declare as a wire an identifier used in a port connection
 - e.g., Q_s
 - Verilog **implicitly declares** identifier as a net of the default net type, typically a *one-bit wire*
 - Intended as shortcut to save typing for large circuits
 - May not give warning message during compilation
 - Works fine if a one-bit wire was desired
 - But may be mismatch – in this example, the wire should have been four bits, not one bit
 - Unexpected simulation results
 - Always explicitly declare wires
 - Best to avoid use of Verilog's implicit declaration shortcut

```
`timescale 1 ns/1 ns
module Testbench();
  reg [3:0] I_s;
  reg Clk_s, Rst_s;
  wire [1:0] Q_s;
  Reg4 CompToTest(I_s, Q_s, Clk_s, Rst_s);
  ...
endmodule
```

11

Finite-State Machines (FSMs)—Sequential Behavior

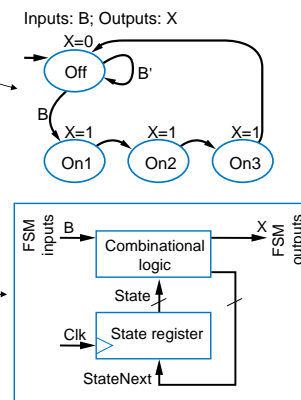- Finite-state machine (FSM) is a common model of sequential behavior
 - Example: If B=1, hold X=1 for 3 clock cycles
 - Note: Transitions implicitly ANDed with rising clock edge
 - Implementation model has two parts:
 - State register
 - Combinational logic
 - HDL model will reflect those two parts



12

Finite-State Machines (FSMs)—Sequential Behavior

Modules with Multiple Procedures and Shared Variables

```

`timescale 1 ns/1 ns
module LaserTimer(B, X, Clk, Rst);
    input B;
    output reg X;
    input Clk, Rst;

    parameter S_Off = 0, S_On1 = 1,
              S_On2 = 2, S_On3 = 3;

    reg [1:0] State, StateNext;

    // CombLogic
    always @(State, B) begin
        case (State)
            S_Off: begin
                X <= 0;
            end
            S_On1: begin
                X <= 1;
            end
            S_On2: begin
                X <= 1;
            end
            S_On3: begin
                X <= 1;
            end
        endcase
    end


    // StateReg
    always @(posedge Clk) begin
        if (Rst == 1)
            State <= S_Off;
        else
            State <= StateNext;
        end
    end
endmodule
    
```

vldd_ch3_LaserTimerBeh.v

13

Finite-State Machines (FSMs)—Sequential Behavior

 - Modules has two procedures
 - One procedure for combinational logic
 - One procedure for state register
 - But it's still a behavioral description



```

`timescale 1 ns/1 ns
module LaserTimer(B, X, Clk, Rst);
    input B;
    output reg X;
    input Clk, Rst;

    parameter S_Off = 0, S_On1 = 1,
              S_On2 = 2, S_On3 = 3;

    reg [1:0] State, StateNext;

    // CombLogic
    always @(State, B) begin
        ...
    end

    // StateReg
    always @(posedge Clk) begin
        ...
    end
endmodule
    
```

vldd_ch3_LaserTimerBeh.v

14

Finite-State Machines (FSMs)—Sequential Behavior

Parameters

- parameter declaration
 - Not a variable or net, but rather a *constant*
 - A constant is a value that must be initialized, and that cannot be changed within the module's definition
 - Four parameters defined
 - S_Off, S_On1, S_On2, S_On3*
 - Correspond to FSM's states
 - Should be initialized to unique values

```

`timescale 1 ns/1 ns
module LaserTimer(B, X, Clk, Rst);
    input B;
    output reg X;
    input Clk, Rst;

    parameter S_Off = 0, S_On1 = 1,
              S_On2 = 2, S_On3 = 3;

    reg [1:0] State, StateNext;

    // CombLogic
    always @(state, B) begin
        ...
    end


    // StateReg
    always @(posedge Clk) begin
        ...
    end
endmodule
    
```

vldd_ch3_LaserTimerBeh.v

15

Finite-State Machines (FSMs)—Sequential Behavior

- Module declares two reg variables
 - State, StateNext*
 - Each is 2-bit vector (need two bits to represent four unique state values 0 to 3)
 - Variables are shared between CombLogic and StateReg procedures
- CombLogic procedure
 - Event control sensitive to *State* and input *B*
 - Will output *StateNext* and *X*
- StateReg procedure
 - Sensitive to *Clk* input
 - Will output *State*, which it stores

 

```

`timescale 1 ns/1 ns
module LaserTimer(B, X, Clk, Rst);
    input B;
    output reg X;
    input Clk, Rst;

    parameter S_Off = 0, S_On1 = 1,
              S_On2 = 2, S_On3 = 3;

    reg [1:0] State, StateNext;

    // CombLogic
    always @(State, B) begin
        ...
    end

    // StateReg
    always @(posedge Clk) begin
        ...
    end
endmodule
    
```

vldd_ch3_LaserTimerBeh.v

16

Finite-State Machines (FSMs)—Sequential Behavior Procedures with Case Statements

Procedure may use case statement

- Preferred over if-else-if when just one expression determines which statement to execute
- case (expression)
 - Execute statement whose case item expression value matches case expression
 - case item expression : statement
 - statement is commonly a begin-end block, as in example
 - First case item expression that matches executes; remaining case items ignored
 - If no item matches, nothing executes
 - Last item may be "default : statement"
 - Statement executes if none of the previous items matched

```
// CombLogic
always @(State, B) begin
  case (State)
    s_Off: begin
      X <= 0;
      if (B == 0)
        StateNext <= s_Off;
      else
        StateNext <= s_On1;
      end
    s_On1: begin
      X <= 1;
      StateNext <= s_On2;
      end
    s_On2: begin
      X <= 1;
      StateNext <= s_On3;
      end
    s_On3: begin
      X <= 1;
      StateNext <= s_Off;
      end
  endcase
end
```

vidd_ch3_LaserTimerBeh.v


17

Finite-State Machines (FSMs)—Sequential Behavior Procedures with Case Statements

FSM's CombLogic procedure

- Case statement describes states
- case (State)
 - Executes corresponding statement (often a begin-end block) based on State's current value
- A state's statements consist of
 - Actions of the state
 - Setting of next state (transitions)

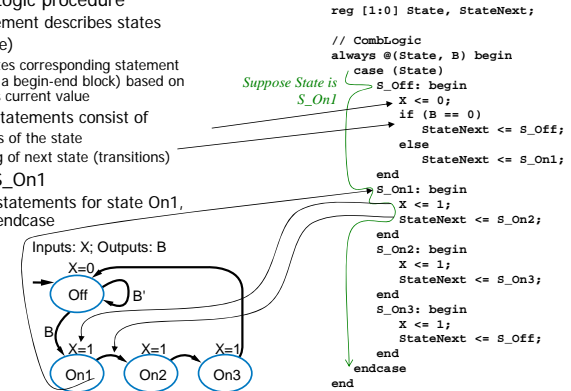- Ex: State is S_On1
- Executes statements for state On1, jumps to endcase



vidd_ch3_LaserTimerBeh.v

18

Finite-State Machines (FSMs)—Sequential Behavior

FSM StateReg Procedure

- Similar to 4-bit register
 - Register for State is 2-bit vector reg variable
- Procedure has synchronous reset
 - Resets State to FSM's initial state, S_Off



```
...
parameter s_Off = 0, s_On1 = 1,
          s_On2 = 2, s_On3 = 3;
...
reg [1:0] State, StateNext;
// StateReg
always @(posedge Clk) begin
  if (Rst == 1)
    State <= s_Off;
  else
    State <= StateNext;
end
...
```

vidd_ch3_LaserTimerBeh.v

19

Finite-State Machines (FSMs)—Sequential Behavior Modules with Multiple Procedures and Shared Variables

Inputs: B; Outputs: X

  

```
`timescale 1 ns/1 ns
module LaserTimer(B, X, Clk, Rst);
  input B;
  output reg X;
  input Clk, Rst;

  parameter s_Off = 0, s_On1 = 1,
            s_On2 = 2, s_On3 = 3;

  reg [1:0] State, StateNext;

  // CombLogic
  always @(State, B) begin
    case (State)
      s_Off: begin
        X <= 0;
        if (B == 0)
          StateNext <= s_Off;
        else
          StateNext <= s_On1;
        end
      s_On1: begin
        X <= 1;
        StateNext <= s_On2;
        end
      s_On2: begin
        X <= 1;
        StateNext <= s_On3;
        end
      s_On3: begin
        X <= 1;
        StateNext <= s_Off;
        end
    endcase
  end


  // StateReg
  always @(posedge Clk) begin
    if (Rst == 1)
      State <= s_Off;
    else
      State <= StateNext;
    end
endmodule
...
```

vidd_ch3_LaserTimerBeh.v

20

Finite-State Machines (FSMs)—Sequential Behavior Self-Checking Testbenches

 - FSM testbench
 - First part of file (variable/net declarations, module instantiations) similar to before
 - Vector Procedure
 - Resets FSM
 - Sets FSM's input values ("test vectors")
 - Waits for specific clock cycles
 - We observe the resulting waveforms to determine if FSM behaves correctly



```
// Clock Procedure
always begin
  Clk_s <= 0;
  #10;
  Clk_s <= 1;
  #10;
end // Note: Procedure repeats


// Vector Procedure
initial begin
  Rst_s <= 1;
  B_s <= 0;
  @(posedge Clk_s);
  #5 Rst_s <= 0;
  @(posedge Clk_s);
  #5 B_s <= 1;
  @(posedge Clk_s);
  #5 B_s <= 0;
  @(posedge Clk_s);
  #5 B_s <= 0;
  @(posedge Clk_s);
  #5 B_s <= 0;
end
endmodule
```

v1dd_ch3_LaserTimerTB.v

21

Finite-State Machines (FSMs)—Sequential Behavior Self-Checking Testbenches

 - Reading waveforms is error-prone
- Create *self-checking testbench*
 - Use *if* statements to check for expected values
 - If a check fails, print error message
 - Ex: if X_s fell to 0 one cycle too early, simulation might output:
 - 95: Third X=1 failed



```
// Vector Procedure
initial begin
  Rst_s <= 1;
  B_s <= 0;
  @(posedge Clk_s);
  #5 if (X_s != 0)
    $display("%t: Reset failed", $time);
  Rst_s <= 0;
  @(posedge Clk_s);
  #5 B_s <= 1;
  @(posedge Clk_s);
  #5 B_s <= 0;
  if (X_s != 1)
    $display("%t: First X=1 failed", $time);
  @(posedge Clk_s);
  #5 if (X_s != 1)
    $display("%t: Second X=1 failed", $time);
  @(posedge Clk_s);
  #5 if (X_s != 1)
    $display("%t: Third X=1 failed", $time);
  @(posedge Clk_s);
  #5 if (X_s != 0)
    $display("%t: Final X=0 failed", $time);
end
```

v1dd_ch3_LaserTimerTBDisplay.v

22

Finite-State Machines (FSMs)—Sequential Behavior \$display System Procedure

- \$display – built-in Verilog system procedure for printing information to display during simulation
 - A *system procedure* interacts with the simulator and/or host computer system
 - To write to a display, read a file, get the current simulation time, etc.
 - Starts with \$ to distinguish from regular procedures
 - String argument is printed literally...
 - \$display("Hello") will print "Hello"
 - Automatically adds newline character
 - ...except when special sequences appear
 - %t: Display a time expression
 - Time expression must be next argument
 - \$time – Built-in system procedure that returns the current simulation time
 - 95: Third X=1 failed

```
// Vector Procedure
initial begin
  Rst_s <= 1;
  B_s <= 0;
  @(posedge Clk_s);
  #5 if (X_s != 0)
    $display("%t: Reset failed", $time);
  Rst_s <= 0;
  @(posedge Clk_s);
  #5 B_s <= 1;
  @(posedge Clk_s);
  #5 B_s <= 0;
  if (X_s != 1)
    $display("%t: First X=1 failed", $time);
  @(posedge Clk_s);
  #5 if (X_s != 1)
    $display("%t: Second X=1 failed", $time);
  @(posedge Clk_s);
  #5 if (X_s != 1)
    $display("%t: Third X=1 failed", $time);
  @(posedge Clk_s);
  #5 if (X_s != 0)
    $display("%t: Final X=0 failed", $time);
end
```

v1dd_ch3_LaserTimerTBDisplay.v

23

Common Pitfall: Not Assigning Every Output in Every State

- FSM outputs should be combinational function of current state (for Moore FSM)
- Not assigning output in given state means previous value is remembered
 - Output has memory
 - Behavior is not an FSM
- Solution 1
 - Be sure to assign every output in every state
- Solution 2
 - Assign default values before case statement
 - Later assignment in state overwrites default

```
// CombLogic
always @(State, B) begin
  X <= 0;
  case (State)
    s_Off: begin
      X <= 0;
      if (B == 0)
        StateNext <= s_Off;
      else
        StateNext <= s_On1;
    end
    s_On1: begin
      X <= 1;
      StateNext <= s_On2;
    end
    s_On2: begin
      X <= 1;
      StateNext <= s_On3;
    end
    s_On3: begin
      X <= 1;
      StateNext <= s_Off;
    end
  endcase
end
```


Could delete this without changing behavior (but probably clearer to keep it)

24

Common Pitfall: Not Assigning Every Output in Every State

o Solution 2

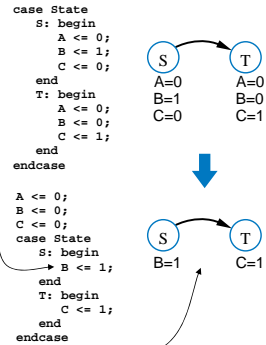- Assign default values before case statement
- Later assignment in state overwrites default
- Helps clarify which actions are important in which state
- Corresponds directly to the common simplifying FSM diagram notation of implicitly setting unassigned outputs to 0



25

The Simulation Cycle

- o Instructive to consider how an HDL simulator works
 - HDL simulation is complex; we'll introduce simplified form
- o Consider example SimEx1
 - Three reg variables – *Q*, *Clk*, *S*
 - Three procedures – P1, P2, P3
- o Simulator's job: Determine values for nets and variables over time
 - Repeatedly executes and suspends procedures
 - o Note: Actually considers more objects, known collectively as *processes*, but we'll keep matters simple here to get just the basic idea of simulation
 - Maintains a simulation time *Time*

```

`timescale 1 ns/1 ns
module SimEx1(Q);
  output reg Q;
  reg Clk, S;

  // P1
  always begin
    Clk <= 0;
    #10;
    Clk <= 1;
    #10;
  end

  // P2
  always @(S) begin
    Q <= ~S;
  end

  // P3
  initial begin
    @(posedge Clk);
    S <= 1;
    @(posedge Clk);
    S <= 0;
  end
endmodule
v1dd_ch3_SimEx1.v


```

26

The Simulation Cycle

o Start of simulation

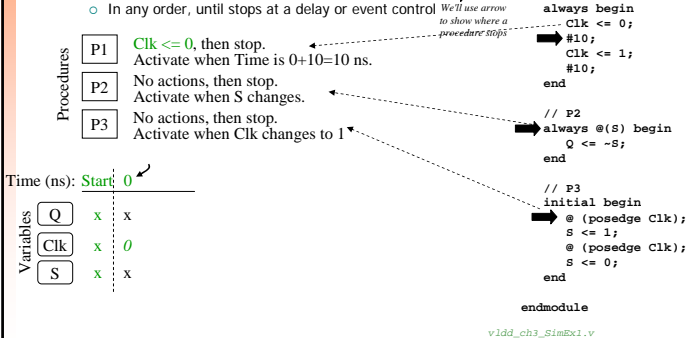- Simulation time *Time* is 0
- Bit variables/nets initialized to the unknown value *x*
- Execute each procedure
 - o In any order, until stops at a delay or event control




27

The Simulation Cycle

o Simulation cycle

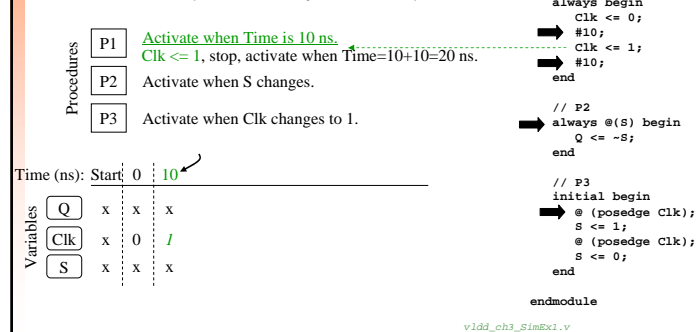- Set time to next time at which a procedure activates (note: could be same as current time)
 - o In this case, time = 10 ns (P1 activates)
- Execute active procedures (in any order) until stops



28

The Simulation Cycle

Simulation cycle

- Set time to next time at which a procedure activates
 - Still 10 ns; Clk just changed to 1 (P3 activates)
- Execute active procedures (in any order) until stops

- Procedures
- P1 Activate when Time is 20 ns.
 - P2 Activate when S changes.
 - P3 Activate when Clk changes to 1.

Time (ns): Start 0 10 10 10

Variables	Q	x	x	x	x
	Clk	x	0	1	1
	S	x	x	x	1

```

`timescale 1 ns/1 ns
module SimEx1(Q);
    output reg Q;
    reg Clk, S;

    // P1
    always begin
        Clk <= 0;
        #10;
        Clk <= 1;
        #10;
    end

    // P2
    always @(S) begin
        Q <= ~S;
    end

    // P3
    initial begin
        @(posedge Clk);
        S <= 1;
        @(posedge Clk);
        S <= 0;
    end
endmodule
    
```

vidd_ch3_SimEx1.v

29

The Simulation Cycle

Simulation cycle

- Set time to next time at which a procedure activates
 - Still 10 ns; S just changed (P2 activates)
- Execute active procedures until stops

- Procedures
- P1 Activate when Time is 20 ns.
 - P2 Activate when S changes.
 - P3 Activate when change on Clk to 1.

Time (ns): Start 0 10 10 10 10

Variables	Q	x	x	x	x	0
	Clk	x	0	1	1	1
	S	x	x	x	1	1

```

`timescale 1 ns/1 ns
module SimEx1(Q);
    output reg Q;
    reg Clk, S;

    // P1
    always begin
        Clk <= 0;
        #10;
        Clk <= 1;
        #10;
    end

    // P2
    always @(S) begin
        Q <= ~S;
    end

    // P3
    initial begin
        @(posedge Clk);
        S <= 1;
        @(posedge Clk);
        S <= 0;
    end
endmodule
    
```

vidd_ch3_SimEx1.v

30

The Simulation Cycle

Simulation cycle

- Set time to next time at which a procedure activates
 - In this case, set Time = 20 ns (P1 activates)
- Execute active procedures until stops

- Procedures
- P1 Activate when Time is 20 ns.
 - P2 Activate when S changes.
 - P3 Activate when change on Clk to 1.

Time (ns): Init 0 10 10 10 10 20

Variables	Q	x	x	x	x	0	0
	Clk	x	0	1	1	1	0
	S	x	x	x	1	1	1

```

`timescale 1 ns/1 ns
module SimEx1(Q);
    output reg Q;
    reg Clk, S;

    // P1
    always begin
        Clk <= 0;
        #10;
        Clk <= 1;
        #10;
    end

    // P2
    always @(S) begin
        Q <= ~S;
    end


    // P3
    initial begin
        @(posedge Clk);
        S <= 1;
        @(posedge Clk);
        S <= 0;
    end
endmodule
    
```

vidd_ch3_SimEx1.v

31

The Simulation Cycle

 - Simulation ends when user-specified time is reached
- Variable/net values translate to waveforms



Time (ns): Init 0 10 10 10 10 20 30 30 40 50

Variables	Q	x	x	x	x	0	0	0	0	1	1	1
	Clk	x	0	1	1	0	1	1	1	0	1	1
	S	x	x	x	1	1	1	0	0	0	0	0

```

`timescale 1 ns/1 ns
module SimEx1(Q);
    output reg Q;
    reg Clk, S;

    // P1
    always begin
        Clk <= 0;
        #10;
        Clk <= 1;
        #10;
    end

    // P2
    always @(S) begin
        Q <= ~S;
    end

    // P3
    initial begin
        @(posedge Clk);
        S <= 1;
        @(posedge Clk);
        S <= 0;
    end
endmodule
    
```

vidd_ch3_SimEx1.v

32

Variable Updates

- Assignment using "<=" ("non blocking assignment") doesn't change variable's value immediately
 - Instead, *schedules* a change of value by placing an *event* on an event queue
 - Scheduled changes occur at end of simulation cycle
 - Important implications
 - Procedure execution order in a simulation cycle doesn't matter
 - Assume procedures 1 and 2 are both active
 - Proc1 schedules B to be 1, *but does not change the present value of B*. B is still 0.
 - Proc2 schedules A to be 0 (the present value of B).
 - At end of simulation cycle, B is updated to 1 and A to 0
 - Order of assignments to different variables in a procedure doesn't matter
 - Assume C was 0. Scheduled values will be C=1 and D=0, for either Proc3a or Proc3b.
 - Later assignment in procedure effectively overwrites earlier assignment
 - E will be updated with 0, but then by 1; so E is 1 at the end of the simulation cycle.

Simulation cycle (revised)

- Set time to next time at which a procedure resumes
- Execute active procedures
- Update variables with schedule values

```
Assume B is 0.
Proc1:
  B <= -B;
Proc2:
  A <= B;
A will be 0, not 1.
```

```
Proc3a: ← Same → Proc3b:
C <= ~C;           D <= C;
D <= C;           C <= ~C;
```

```
Proc4:
  E <= 0;
  ...
  E <= 1;
```

Recall FSM output assignment example, in which default assignments were added before the case statement.